
Jean-Pierre Deschamps • Elena Valderrama
Lluís Terés

Digital Systems

From Logic Gates to Processors

 Springer

Contents

1	Digital Systems	1
1.1	Definition	1
1.2	Description Methods	4
1.2.1	Functional Description	4
1.2.2	Structural Description	7
1.2.3	Hierarchical Description	8
1.3	Digital Electronic Systems	10
1.3.1	Real System Structure	10
1.3.2	Electronic Components	11
1.3.3	Synthesis of Digital Electronic Systems	18
1.4	Exercises	18
	References	20
2	Combinational Circuits	21
2.1	Definitions	21
2.2	Synthesis from a Table	22
2.3	Boolean Algebra	27
2.3.1	Definition	27
2.3.2	Some Additional Properties	30
2.3.3	Boolean Functions and Truth Tables	31
2.3.4	Example	34
2.4	Logic Gates	35
2.4.1	NAND and NOR	35
2.4.2	XOR and XNOR	37
2.4.3	Tristate Buffers and Tristate Inverters	41
2.5	Synthesis Tools	42
2.5.1	Redundant Terms	42
2.5.2	Cube Representation	45
2.5.3	Adjacency	47
2.5.4	Karnaugh Map	48
2.6	Propagation Time	50
2.7	Other Logic Blocks	55
2.7.1	Multiplexers	55
2.7.2	Multiplexers and Memory Blocks	58
2.7.3	Planes	60
2.7.4	Address Decoder and Tristate Buffers	60

2.8	Programming Language Structures	62
2.8.1	If Then Else	62
2.8.2	Case	63
2.8.3	Loops	63
2.8.4	Procedure Calls	65
2.8.5	Conclusion	66
2.9	Exercises	66
	References	67
3	Arithmetic Blocks	69
3.1	Binary Adder	69
3.2	Binary Subtractor	70
3.3	Binary Adder/Subtractor	71
3.4	Binary Multiplier	72
3.5	Binary Divider	74
3.6	Exercises	76
	References	77
4	Sequential Circuits	79
4.1	Introductory Example	79
4.2	Definition	80
4.3	Explicit Functional Description	83
4.3.1	State Transition Graph	83
4.3.2	Example of Explicit Description Generation	86
4.3.3	Next State Table and Output Table	88
4.4	Bistable Components	88
4.4.1	1-Bit Memory	89
4.4.2	Latches and Flip-Flops	91
4.5	Synthesis Method	93
4.6	Sequential Components	96
4.6.1	Registers	97
4.6.2	Counters	101
4.6.3	Memories	107
4.7	Sequential Implementation of Algorithms	113
4.7.1	A First Example	113
4.7.2	Combinational vs. Sequential Implementation	116
4.8	Finite-State Machines	119
4.8.1	Definition	119
4.8.2	VHDL Model	121
4.9	Examples of Finite-State Machines	126
4.9.1	Programmable Timer	126
4.9.2	Sequence Recognition	129
4.10	Exercises	132
	References	133

5	Synthesis of a Processor	135
5.1	Definition	135
5.1.1	Specification	135
5.1.2	Design Strategy	136
5.2	Functional Specification	143
5.2.1	Instruction Types	143
5.2.2	Specification	143
5.3	Structural Specification	145
5.3.1	Block Diagram	145
5.3.2	Component Specification	147
5.4	Component Implementation	150
5.4.1	Input Selection Component	150
5.4.2	Computation Resources	152
5.4.3	Output Selection	153
5.4.4	Register Bank	155
5.4.5	Go To Component	158
5.5	Complete Processor	160
5.5.1	Instruction Encoding	160
5.5.2	Instruction Decoder	161
5.5.3	Complete Circuit	161
5.6	Test	164
	References	170
6	Design Methods	171
6.1	Structural Description	171
6.2	RTL Behavioral Description	172
6.3	High-Level Synthesis Tools	175
	References	177
7	Physical Implementation	179
7.1	Manufacturing Technologies	179
7.2	Implementation Strategies	184
7.2.1	Standard Cell Approach	184
7.2.2	Mask Programmable Gate Arrays	185
7.2.3	Field Programmable Gate Arrays	185
7.3	Synthesis and Physical Implementation Tools	188
	References	188
	Appendix A: A VHDL Overview	189
	Appendix B: Pseudocode Guidelines for the Description of Algorithms	217
	Appendix C: Binary Numeration System	227
	Index	237