

Digital Design

with RTL Design, VHDL, and Verilog

SECOND EDITION



Frank Vahid

Obra protegida por Direitos de Autor

Digital Design

with RTL Design, VHDL, and Verilog

SECOND EDITION

FRANK VAHID

University of California, Riverside

 **WILEY**

A John Wiley & Sons, Inc., Publication

*To my family, Amy, Eric, Kelsi, and Maya;
and to all engineers who apply their skills
to improve the human condition.*

VP and EXECUTIVE PUBLISHER	Don Fowley
ASSOCIATE PUBLISHER	Dan Sayre
EDITORIAL ASSISTANT	Katie Singleton
SENIOR PRODUCTION MANAGER	Micheline Frederick
SENIOR PRODUCTION EDITOR	Kerry Weinstein
EXECUTIVE MARKETING MANAGER	Christopher Ruel
COVER DESIGNER	Jim O'Shea
MEDIA EDITOR	Lauren Sapira
COVER PHOTO	Comstock Images/Getty Images, Inc.; iStockphoto

This book was set in 10/12 Times Roman by Frank Vahid. The text and cover were printed by Donnelley/Crawfordsville.

Copyright © 2011, 2007 John Wiley & Sons, Inc. All rights reserved. No part of this publication may be reproduced, stored in a retrieval system or transmitted in any form or by any means, electronic, mechanical, photocopying, recording, scanning or otherwise, except as permitted under Sections 107 or 108 of the 1976 United States Copyright Act, without either the prior written permission of the Publisher, or authorization through payment of the appropriate per-copy fee to the Copyright Clearance Center, Inc. 222 Rosewood Drive, Danvers, MA 01923, website www.copyright.com. Requests to the Publisher for permission should be addressed to the Permissions Department, John Wiley & Sons, Inc., 111 River Street, Hoboken, NJ 07030-5774, (201)748-6011, fax (201)748-6008, website <http://www.wiley.com/go/permissions>.

Evaluation copies are provided to qualified academics and professionals for review purposes only, for use in their courses during the next academic year. These copies are licensed and may not be sold or transferred to a third party. Upon completion of the review period, please return the evaluation copy to Wiley. Return instructions and a free of charge return shipping label are available at www.wiley.com/go/returnlabel. Outside of the United States, please contact your local representative.

ISBN 978-0-470-53108-2

Printed in the United States of America
10 9 8 7 6 5 4 3 2 1

Contents

Preface ix

To Students About To Study Digital Design ix

To Instructors of Digital Design ix

How to Use This Book xii

RTL-Focused Approach xii

Traditional Approach with Some Reordering xii

Traditional Approach xiii

Acknowledgements xiii

About the Cover xiv

About the Author xiv

Reviewers and Evaluators xv

► CHAPTER 1

Introduction 1

1.1 Digital Systems in the World Around Us 1

1.2 [The World of Digital Systems 4](#)

[Digital versus Analog 4](#)

Digital Encodings and Binary Numbers—0s and 1s 9

1.3 Implementing Digital Systems:

Microprocessors versus Digital Circuits 22

Software on Microprocessors: The Digital Workhorse 22

Digital Design—When Microprocessors Aren't Good Enough 26

1.4 [About this Book 28](#)

1.5 Exercises 29

► CHAPTER 2

Combinational Logic Design 35

2.1 Introduction 35

2.2 Switches 36

Electronics 101 36

The Amazing Shrinking Switch 37

2.3 [The CMOS Transistor 40](#)

2.4 Boolean Logic Gates—Building Blocks for Digital Circuits 43

Boolean Algebra and its Relation to Digital Circuits 43

AND, OR, & NOT Gates 46

Building Simple Circuits Using Gates 49

2.5 [Boolean Algebra 52](#)

Notation and Terminology 53

Some Properties of Boolean Algebra 55

Complementing a Function 60

2.6 Representations of Boolean Functions 61

Equations 62

Circuits 62

Truth Tables 62

[Converting among Boolean Function Representations 64](#)

[Standard Representation and Canonical Form 68](#)

Multiple-Output Combinational Circuits 71

2.7 Combinational Logic Design Process 73

2.8 [More Gates 80](#)

[NAND & NOR 80](#)

XOR & XNOR 81

Interesting Uses of these Additional Gates 82

Completeness of NAND and of NOR 82

Number of Possible Logic Gates 83

2.9 Decoders and Muxes 84

Decoders 84

Multiplexers (Muxes) 86

2.10 Additional Considerations 91

Nonideal Gate Behavior—Delay 91

Active Low Inputs 92

Demultiplexers and Encoders 93

Schematic Capture and Simulation 93

2.11 Combinational Logic Optimizations and Tradeoffs (See Section 6.2) 95

2.12 Combinational Logic Description Using Hardware Description Languages (See Section 9.2) 95

2.13 Chapter Summary 96

2.14 Exercises 96

iv ► Contents

► **CHAPTER 3****Sequential Logic Design: Controllers 105****3.1 Introduction 105****3.2 Storing One Bit—Flip-Flops 106**Feedback—The Basic Storage Method 106Basic SR Latch 107Level-Sensitive SR Latch 111Level-Sensitive D Latch—A Basic Bit Store 112Edge-Triggered D Flip-Flop—A Robust Bit Store 113Clocks and Synchronous Circuits 117Basic Register—Storing Multiple Bits 120**3.3 Finite-State Machines (FSMs) 122**Mathematical Formalism for Sequential Behavior—FSMs 124How to Capture Desired System Behavior as an FSM 129**3.4 Controller Design 132**Standard Controller Architecture for Implementingan FSM as a Sequential Circuit 132Controller (Sequential Logic) Design Process 133Converting a Circuit to an FSM (Reverse Engineering) 140Common Mistakes when Capturing FSMs 142FSM and Controller Conventions 145**3.5 More on Flip-Flops and Controllers 146**Non-Ideal Flip-Flop Behavior 146Flip-Flop Reset and Set Inputs 149Initial State of a Controller 150Non-Ideal Controller Behavior: Output Glitches 151**3.6 Sequential Logic Optimizations and Tradeoffs**(See Section 6.3) 153**3.7 Sequential Logic Description Using**Hardware Description Languages (See Section 9.3) 153**3.8 Product Profile—Pacemaker 153****3.9 Chapter Summary 156****3.10 Exercises 157**► **CHAPTER 4****Datapath Components 167****4.1 Introduction 167****4.2 Registers 168**Parallel-Load Register 168Shift Register 173Multifunction Registers 175Register Design Process 179**4.3 Adders 181**Adder—Carry-Ripple Style 183**4.4 Comparators 191**Equality (Identity) Comparator 191Magnitude Comparator—Carry-Ripple Style 192**4.5 Multiplier—Array-Style 195****4.6 Subtractors and Signed Numbers 196**Subtractor for Positive Numbers Only 196Representing Negative Numbers: Two'sComplement Representation 200Building a Subtractor Using an Adder and Two's Complement 203Detecting Overflow 205**4.7 Arithmetic-Logic Units—ALUs 207****4.8 Shifters 210**Simple Shifters 211Barrel Shifter 214**4.9 Counters and Timers 215**Up-Counter 216Up/Down-Counter 217Counter with Load 218Timers 222**4.10 Register Files 225****4.11 Datapath Component Tradeoffs (See Section 6.4) 230****4.12 Datapath Component Description Using Hardware Description Languages (See Section 9.4) 230****4.13 Product Profile: An Ultrasound Machine 230**Functional Overview 231Digital Circuits in an Ultrasound Machine's Beamformer 234Future Challenges in Ultrasound 237**4.14 Chapter Summary 237****4.15 Exercises 238**

▶ CHAPTER 5**Register-Transfer Level (RTL) Design 247**

- 5.1** Introduction 247
- 5.2** High-Level State Machines 248
- 5.3** RTL Design Process 255
 - Step 2A—Creating a Datapath using Components from a Library 259
 - Step 2B—Connecting the Datapath to a Controller 262
 - Step 2C—Deriving the Controller's FSM 263
- 5.4** More RTL Design 264
 - Additional Datapath Components for the Library 264
 - RTL Design Involving Register Files or Memories 265
 - RTL Design Pitfall Involving Storage Updates 271
 - RTL Design Involving a Timer 272
 - A Data-Dominated RTL Design Example 275
- 5.5** Determining Clock Frequency 278
- 5.6** Behavioral-Level Design: C to Gates (Optional) 281
- 5.7** Memory Components 285
 - Random Access Memory (RAM) 286
 - Bit Storage in a RAM 288
 - Using a RAM 290
 - Read-Only Memory (ROM) 292
 - ROM Types 294
 - Using a ROM 297
 - The Blurring of the Distinction between RAM and ROM 299
- 5.8** Queues (FIFOs) 299
- 5.9** Multiple Processors 303
- 5.10** Hierarchy—A Key Design Concept 305
 - Managing Complexity 305
 - Abstraction 306
 - Composing a Larger Component from Smaller Versions of the Same Component 307
- 5.11** RTL Design Optimizations and Tradeoffs (See Section 6.5) 309
- 5.12** RTL Design Using Hardware Description Languages (See Section 9.5) 310

5.13 Product Profile: Cell Phone 310

- Cells and Basestations 310
- How Cellular Phone Calls Work 311
- Inside a Cell Phone 312

5.14 Chapter Summary 316**5.15 Exercises 317****▶ CHAPTER 6****Optimizations and Tradeoffs 325**

- 6.1** Introduction 325
- 6.2** Combinational Logic Optimizations and Tradeoffs 327
 - Two-Level Size Optimization Using Algebraic Methods 327
 - A Visual Method for Two-Level Size Optimization—K-Maps 329
 - Don't Care Input Combinations 336
 - Automating Two-Level Logic Size Optimization 339
 - Multilevel Logic Optimization—Performance and Size Tradeoffs 348
- 6.3** Sequential Logic Optimizations and Tradeoffs 351
 - State Reduction 351
 - State Encoding 354
 - Moore versus Mealy FSMs 360
- 6.4** Datapath Component Tradeoffs 365
 - Faster Adders 365
 - Smaller Multiplier—Sequential (Shift-and-Add) Style 375
- 6.5** RTL Design Optimizations and Tradeoffs 377
 - Pipelining 377
 - Concurrency 380
 - Component Allocation 381
 - Operator Binding 382
 - Operator Scheduling 383
 - Moore versus Mealy High-Level State Machines 386
- 6.6** More on Optimizations and Tradeoffs 386
 - Serial versus Concurrent Computation 386
 - Optimizations and Tradeoffs at Higher versus Lower Levels of Design 387
 - Algorithm Selection 388
 - Power Optimization 389

[vi ▶ Contents](#)

- 6.7 Product Profile: Digital Video Player/Recorder 393**
 - Digital Video Overview 393
 - DVD—One Form of Digital Video Storage 393
 - MPEG-2 Video Encoding—Sending Frame Differences Using I-, P-, and B-Frames 395
 - Transforming to the Frequency Domain for Further Compression 396
- 6.8 Chapter Summary 402**
- 6.9 Exercises 403**

▶ CHAPTER 7

Physical Implementation on ICs 413

- 7.1 Introduction 413**
- 7.2 Manufactured IC Types 414**
 - Full-Custom Integrated Circuits 414
 - Semicustom (Application-Specific) Integrated Circuits—ASICs 415
- 7.3 Off-the-Shelf Programmable IC Type—FPGA 423**
 - Lookup Tables 424
 - Mapping a Circuit among Multiple Lookup Tables 426
 - Programmable Interconnects (Switch Matrices) 432
 - Configurable Logic Block 434
 - Overall FPGA Architecture 436
- 7.4 Other Off-the-Shelf IC Types 438**
 - Off-the-Shelf Logic (SSI) IC 438
 - Simple Programmable Logic Device (SPLD) 441
 - Complex Programmable Logic Device (CPLD) 445
 - FPGA-to-Structured-ASIC Flows 445
- 7.5 IC Tradeoffs, Trends, and Comparisons 446**
 - Tradeoffs Among IC Types 447
 - IC Technology Trend—Moore’s Law 448
 - Relative Popularity of IC Types 450
 - ASSPs 450
 - IC Types versus Processor Varieties 451
 - FPGAs alongside Microprocessors 452
- 7.6 Product Profile: Giant LED-Based Video Display with FPGAs 453**
- 7.7 Chapter Summary 457**
- 7.8 Exercises 457**

▶ CHAPTER 8

Programmable Processors 461

- 8.1 Introduction 461**
- 8.2 Basic Architecture 462**
 - Basic Datapath 462
 - Basic Control Unit 465
- 8.3 A Three-Instruction Programmable Processor 469**
 - A First Instruction Set with Three Instructions 469
 - Control Unit and Datapath for the Three-Instruction Processor 471
- 8.4 A Six-Instruction Programmable Processor 475**
 - Extending the Instruction Set 475
 - Extending the Control Unit and Datapath 476
- 8.5 Example Assembly and Machine Programs 478**
- 8.6 Further Extensions to the Programmable Processor 480**
 - Instruction Set Extensions 480
 - Input/Output Extensions 481
 - Performance Extensions 481
- 8.7 Chapter Summary 482**
- 8.8 Exercises 483**

▶ CHAPTER 9

Hardware Description Languages 487

- 9.1 Introduction 487**
- 9.2 Combinational Logic Description Using Hardware Description Languages 489**
 - Structure 489
 - Combinational Behavior 494
 - Testbenches 498
- 9.3 Sequential Logic Description Using Hardware Description Languages 501**
 - Register 501
 - Oscillator 503
 - Controllers 505
- 9.4 Datapath Component Description Using Hardware Description Languages 509**
 - Full-Adders 509

- Carry-Ripple Adders 511
- Up-Counter 514
- 9.5** RTL Design Using Hardware Description Languages 517
- High-Level State Machine of the Laser-Based Distance Measurer 517
- Controller and Datapath of the Laser-Based Distance Measurer 523
- 9.6** Chapter Summary 532
- 9.7** Exercises 532

▶ **APPENDIX A**

- Boolean Algebras 537
- A.1** Boolean Algebra 537
- A.2** Switching Algebra 538
- A.3** Important Theorems in Boolean Algebra 540
- A.4** Other Examples of Boolean Algebras 545
- A.5** Further Readings 545

▶ **APPENDIX B**

Additional Topics in Binary Number Systems 547

- B.1** Introduction 547
- B.2** Real Number Representation 547
- B.3** Fixed Point Arithmetic 550
- B.4** Floating Point Representation 551
- The IEEE 754-1985 Standard 552
- B.5** Exercises 556

▶ **APPENDIX C**

Extended RTL Design Example 557

- C.1** Introduction 557
- C.2** Designing the Soda Dispenser Controller 558
- C.3** Understanding the Behavior of the Soda Dispenser Controller and Datapath 562



*image
not
available*

*image
not
available*

*image
not
available*

4 ► 1 Introduction

► 1.2 THE WORLD OF DIGITAL SYSTEMS

Digital versus Analog

A **digital** signal, also known as a discrete signal, is a signal that at any time can have one of a finite set of possible values. In contrast, an **analog** signal can have one of an infinite number of possible values, and is also known as a continuous signal. A signal is just some physical phenomenon that has a unique value at every instant of time. An everyday example of an analog signal is the temperature outside, because physical temperature is a continuous value—the temperature may be 92.356666... degrees. An everyday example of a digital signal is the number of fingers you hold up, because the value must be either 0, 1, 2, 3, 4, 5, 6, 7, 8, 9, or 10—a finite set of values. In fact, the term “digital” comes from the Latin word for “digit” (*digitus*), meaning finger.

In computing systems, the most common digital signals are those that can have one of only two possible values, like on or off (often represented as 1 or 0). Such a two-valued representation is known as a **binary** representation. A **digital system** is a system that takes digital inputs and generates digital outputs. A **digital circuit** is a connection of digital components that together comprise a digital system. In this textbook, the term “digital” will refer to systems with binary-valued signals. A single binary signal is known as a binary digit, or **bit** for short (*binary digit*). Digital electronics became extremely popular in the mid-1900s after the invention of the transistor, an electric switch that can be turned on or off using another electric signal. We’ll describe transistors further in the next chapter.



Figure 1.1 (a) General-purpose computer



(b) Embedded systems

About 100,000 unique new digital circuits were designed in 2008.

Digital Circuits are the Basis for Computers

The most well-known use of digital circuits in the world around us is probably to build the microprocessors that serve as the brain of general-purpose computers, like the personal computer or laptop computer that you might have at home, illustrated in Figure 1.1(a). General-purpose computers are also used as servers, which operate behind the scenes to implement banking, airline reservation, web search, payroll, and similar such systems. General-purpose computers take digital input data, such as letters and numbers received from files or keyboards, and output new digital data, such as new letters and numbers stored in files or displayed on a monitor. Learning about digital design is therefore useful in understanding how computers work “under the hood,” and hence has been required learning for most computing and electrical engineering majors for decades. Based on material in upcoming chapters, we’ll design a simple computer in Chapter 8.

Digital Circuits are the Basis for Much More

Increasingly, digital circuits are being used for much more than implementing general-purpose computers. More and more new applications convert analog signals to digital ones, and run those digital signals through customized digital circuits, to achieve numerous benefits. Such applications, such as those in Figure 1.1(b), include cell phones, automobile engine controllers, TV set-top boxes, music instruments, digital cameras and camcorders, video game consoles, and so on. Digital circuits found inside applications other than general-purpose computers are often called **embedded systems**, because those digital systems are embedded inside another electronic device.

*image
not
available*

*image
not
available*

*image
not
available*

8 ► 1 Introduction

 


Figure 1.4 More and more analog products are becoming primarily digital.

Figure 1.4, over the past decade numerous products that were previously analog have converted primarily to digital technology. Portable music players, for example, switched from cassette tapes to digital CDs in the middle 1990s, and recently to MP3s and other digital formats. Early cell phones used analog communication, but in the late 1990s digital communication, similar in idea to that shown in Figure 1.3, became dominant. In the early 2000s, analog VHS video players gave way to digital video disc (DVD) players, and then to hard-drive-based digital video recorders (DVRs). Portable video cameras have begun to digitize video before storing the video onto tape or a hard drive, while still picture cameras have eliminated film and store photos on digital cards. Musical instruments are increasingly digital-based, with electronic drums, keyboards, and electric guitars including more digital processing. Analog TV is also giving way to digital TV. Hundreds of other devices have converted from analog to digital in past decades, such as clocks and watches, household thermostats, human temperature thermometers (which now work in the ear rather than under the tongue or other places), car engine controllers, gasoline pumps, hearing aids, and more. Many other devices were never analog, instead being introduced in digital form from the very start. For example, video games have been digital since their inception.

The above devices use digitization, and digitization requires that phenomena be encoded into 1s and 0s. Computations using digital circuits also require that numbers be digitized into 1s and 0s. The next section describes how to encode items digitally.

► THE TELEPHONE.

The telephone, patented by Alexander Graham Bell in the late 1800s (though invented by Antonio Meucci), operates using the electromagnetic principle described earlier—your speech creates sound waves that move a membrane, which moves a magnet, which creates current on a nearby wire. Run that wire to somewhere far away, put a magnet connected to a membrane near that wire, and the membrane will move, producing sound waves that sound like you talking. Much of the telephone system today digitizes the audio to improve quality and quantity of audio transmissions over long distances. A couple of interesting facts about the telephone:

- Believe it or not, Western Union actually turned down Bell's initial proposal to develop the telephone, perhaps thinking that the then-popular

telegraph was all people needed.

- Bell and his assistant Watson disagreed on how to answer the phone: Watson wanted "Hello," which won, but Bell wanted "Hoy hoy" instead. (Fans of the TV show *The Simpsons* may have noticed that Homer's boss, Mr. Burns, answers the phone with a "hoy hoy.")



An early-style telephone.

(Source of some of the above material: www.pbs.org, transcript of "The Telephone").

*image
not
available*

*image
not
available*

*image
not
available*

12 ► 1 Introduction

► NAMES IN BASE TEN.

Indian English has a name for 10^5 : lakh. In 2008, the Indian car company Tata Motors unveiled the “one lakh car,” costing a mere 100,000 rupees, or about \$2,500.

The Web search tool name Google comes from the word “googol”—a 1 followed by 100 zeroes, apparently implying that the tool can search a lot of information.

English speakers use names for various quantities in base ten, names that are useful but can hamper gaining an intuitive understanding of base ten. 10^2 has its own name: *hundred*. 10^3 has the name *thousand*. There is no name (in American English) for 10^4 or 10^5 . 10^6 has the name *million*, and subsequent groups that are multiples of 1,000 have the names *billion*, *trillion*, *quadrillion*, etc. English speakers also use abbreviated names for groups of tens—the numbers 10, 20, 30, ..., 90 could be called one ten, two ten, up to nine ten, but instead have abbreviated names: one ten as just “ten,” two ten is “twenty,” up to nine ten being “ninety.” You can see how “ninety” is a shortening of “nine ten.” Special names are also used for the numbers between 10 and 20. 11 could be “one ten one,” but is instead “eleven,” while 19 could be “one ten nine” but is

instead “nineteen.” Table 1.1 indicates how one might count in base ten without these various names, to emphasize the nature of base ten. 523 might be spoken as “five hundred two ten three” rather than “five hundred twenty-three.” Kids may have a harder time learning math because of the arbitrary base ten names—for example, carrying a one from the ones column to the tens column makes more sense if the ones column sums to “one ten seven” rather than to “seventeen”—“one ten seven” obviously adds one to the tens column. Likewise, learning binary may be slightly harder for some students due to a lack of a solid understanding of base ten. To help remedy the situation, perhaps when a store clerk tells you “That will be ninety-nine cents,” you might say “You mean nine ten nine cents.” If enough of us do this, perhaps it will catch on?

Table 1.1 Counting in base ten without the abbreviated or short names.

0 to 9	As usual: “zero,” “one,” “two,” ..., “nine.”
10 to 99	10, 11, 12, ... 19: “one ten,” “one ten one,” “one ten two,” ... “one ten nine” 20, 21, 22, ..., 29: “two ten,” “two ten one,” “two ten two,” ... “two ten nine” 30, 40, ... 90: “three ten,” “four ten,” ... “nine ten”
100 to 900	As usual: “one hundred,” “two hundred,” ... “nine hundred.” Even clearer would be to replace the word “hundred” by “ten to the power of 2.”
1000 and up	As usual. Even clearer for understanding bases: replace “thousand” by “ten to the (power of) 3,” “ten thousand” by “ten to the 4,” etc., eliminating the various names.

Example 1.1 Using digital data in a digital system

A digital system is desired that reads the value of a temperature sensor and shows the letter “F” (for “freezing”) on a display if the temperature is 32 degrees Fahrenheit or below, shows “N” (for “normal”) if the temperature is between 32 and 212 degrees, and shows the letter “B” (for “boiling”) if the temperature is 212 or greater. The temperature sensor has an 8-bit output representing the temperature as a binary number between 0 and 255. The display has a 7-bit input that accepts an ASCII bit encoding and displays the corresponding symbol.

Figure 1.13 shows the temperature sensor output connected to the input of the desired digital system. Each wire can have

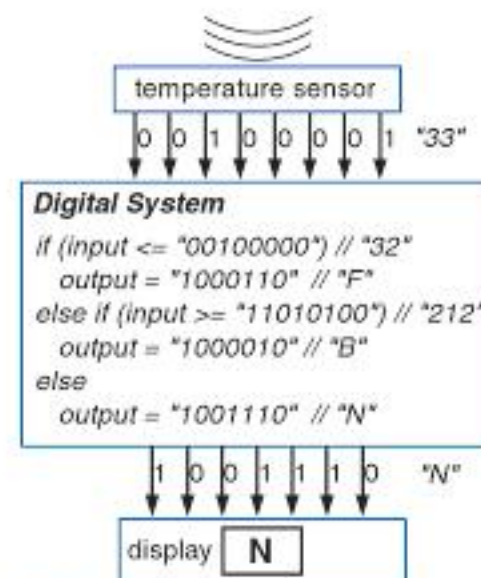


Figure 1.13 Digital system with bit encoded input (an 8-bit binary number) and 7-bit output (ASCII). The desired behavior of the digital system is shown.

*image
not
available*

*image
not
available*

*image
not
available*

 


Figure 1.17 Decimal to binary conversion for a DIP switch: (a) ceiling fan with remote control, both having DIP switches to set their communication channel, (b) setting the fan's channel to "73" requires first converting 73 to binary, then setting the DIP switch to represent that binary value, (c) ceiling fan module only outputs 1 if the received channel matches DIP switch setting.

Instead, he/she can open the ceiling fan module and the remote controller of one pair, and simply change the DIP switch settings for that pair, ensuring that both DIP switches match after the change.

While this section introduced the addition method for converting from decimal to binary, many books and web resources introduce the **subtraction method**, wherein we start by setting a current number to the desired decimal number, put a 1 in the highest binary number place that doesn't exceed the current number, subtract that place's weight from the current number, and repeat until the current number reaches zero. The two methods are fundamentally the same; the addition method may be more intuitive when converting by hand.

Hexadecimal and Octal Numbers

Base sixteen numbers, known as **hexadecimal numbers** or just **hex**, are also popular in digital design, mainly because one base sixteen digit is equivalent to four base two digits, making hexadecimal numbers a nice shorthand representation for binary numbers. In base sixteen, the first digit represents up to fifteen ones—the sixteen symbols commonly used are 0, 1, 2, ..., 9, A, B, C, D, E, F (so A = ten, B = eleven, C = twelve, D = thirteen, E = fourteen, and F = fifteen). The next digit represents the number of groups of 16^1 , the next digit the number of groups of 16^2 , etc., as shown in Figure 1.18. So $8AF_{16}$ equals $8 \cdot 16^2 + 10 \cdot 16^1 + 15 \cdot 16^0$, or 2223_{10} .

*image
not
available*

*image
not
available*

*image
not
available*

	Decimal	Binary
1. Divide decimal number by 2 Insert remainder into the binary number Continue since quotient (6) is greater than 0	$\begin{array}{r} 6 \\ 2 \overline{)12} \\ \underline{-12} \\ 0 \end{array}$	$\begin{array}{c} 0 \\ 1 \end{array}$ (current value: 0)
2. Divide quotient by 2 Insert remainder into the binary number Continue since quotient (3) is greater than 0	$\begin{array}{r} 3 \\ 2 \overline{)6} \\ \underline{-6} \\ 0 \end{array}$	$\begin{array}{cc} 0 & 0 \\ 2 & 1 \end{array}$ (current value: 0)
3. Divide quotient by 2 Insert remainder into the binary number Continue since quotient (1) is greater than 0	$\begin{array}{r} 1 \\ 2 \overline{)3} \\ \underline{-2} \\ 1 \end{array}$	$\begin{array}{ccc} 1 & 0 & 0 \\ 4 & 2 & 1 \end{array}$ (current value: 4)
4. Divide quotient by 2 Insert remainder into the binary number Quotient is 0, done	$\begin{array}{r} 0 \\ 2 \overline{)1} \\ \underline{-0} \\ 1 \end{array}$	$\begin{array}{cccc} 1 & 1 & 0 & 0 \\ 8 & 4 & 2 & 1 \end{array}$ (current value: 12)

Figure 1.21 Converting the decimal number 12 to binary using the divide-by-2 method.

1110. Checking the answer shows that 1110 is correct: $1 \cdot 2^3 + 1 \cdot 2^2 + 1 \cdot 2^1 + 0 \cdot 2^0 = 8 + 4 + 2 + 0 = 14$.

To convert 99 to binary, the process is the same but naturally takes more steps: $99/2 = 49$ remainder 1. $49/2 = 24$, remainder 1. $24/2 = 12$, remainder 0. $12/2 = 6$, remainder 0. $6/2 = 3$, remainder 0. $3/2 = 1$, remainder 1. $1/2 = 0$, remainder 1. Combining the remainders together gives us the binary number 1100011. We know from Example 1.3 that this is the correct answer.

We can use the same basic method to convert a base 10 number to a number in *any* base. To convert a number from base 10 to base n , we repeatedly divide the number by n and place the remainder in the new base n number, starting from the least significant digit. The method is called the *divide-by- n method*.

Example 1.9 Decimal to arbitrary bases using the divide-by- n method

Convert the number 3439 to base 10 and to base 7.

We know the number 3439 is 3439 in base 10, but let's use the divide-by- n method (where n is 10) to illustrate that the method works for any base. We start by dividing 3439 by 10: $3439/10 = 343$, remainder 9. We then divide the quotient by 10: $343/10 = 34$, remainder 3. We do the same with the new quotient: $34/3 = 3$, remainder 4. Finally, we divide 3 by 10: $3/10 = 0$, remainder 3. Combining the remainders, least significant digit first, gives us the base 10 number 3439.

To convert 3439 to base 7, the approach is similar, except we now divide by 7. We begin by dividing 3439 by 7: $3439/7 = 491$, remainder 2. Continuing our calculations, we get $491/7 = 70$, remainder 1. $70/7 = 10$, remainder 0. $10/7 = 1$, remainder 3. $1/7 = 0$, remainder 1. Thus, 3439 in base 7 is 13012. Checking the answer verifies that we have the correct result: $1 \cdot 7^4 + 3 \cdot 7^3 + 0 \cdot 7^2 + 1 \cdot 7^1 + 2 \cdot 7^0 = 2401 + 1029 + 7 + 2 = 3439$.

Conversion between any two bases can be done by first converting to base ten, then converting the base ten number to the desired base using the divide-by- n method.

*image
not
available*

*image
not
available*

*image
not
available*

24 ► 1 Introduction

Figure 1.25 shows an example of the values of signals a , b , and F over time, with time proceeding to the right. As time proceeds, each signal may be either 0 or 1, illustrated by each signal's associated line being either low or high. We made a equal to 0 until time 7:05, when we made a become 1. We made a stay 1 until 7:06, when we made a return back to 0. We made a stay 0 until 9:00, when we made a become 1 again, and then we made a become 0 at 9:01. On the other hand, we made b start as 0, and then become 1 between 7:06 and 9:00. The diagram shows what the value of F would be given the C program executing on the microprocessor—when a is 1 and b is 0 (from 7:05 to 7:06), F will be 1. A diagram with time proceeding to the right, and the values of digital signals shown by high or low lines, is known as a **timing diagram**. We draw the input lines (a and b) to be whatever values we want, but then the output line (F) must describe the behavior of the digital system.

 


Figure 1.25 Timing diagram of motion-in-the-dark detector system.

Example 1.10 Outdoor motion notifier using a microprocessor

Let's use the basic microprocessor of Figure 1.23 to implement a system that sounds a buzzer when motion is detected at any of three motion sensors outside a house. We connect the motion sensors to microprocessor input pins $I0$, $I1$, and $I2$, and connect output pin $P0$ to a buzzer (Figure 1.26). (We assume the motion sensors and buzzers have appropriate electronic interfaces to the microprocessor pins.) We can then write the following C program:

```
void main()
{
    while (1) {
        P0 = I0 || I1 || I2;
    }
}
```

The program executes the statement inside the while loop repeatedly. That statement will set $P0$ to 1 if $I0$ is 1 or (written as $||$ in the C language) $I1$ is 1 or $I2$ is 1, otherwise the statement sets $P0$ to 0.

 


Figure 1.26 Motion sensors connected to microprocessor.

*image
not
available*

*image
not
available*

*image
not
available*

*image
not
available*

*image
not
available*

*image
not
available*

*image
not
available*

32 ► 1 Introduction

1.22 Convert the following hexadecimal numbers to binary:

- (a) 4F5E
- (b) 3FAD
- (c) 3E2A
- (d) DEED

1.23 Convert the following hexadecimal numbers to binary:

- (a) B0C4
- (b) 1EF03
- (c) F002
- (d) BEEF

1.24 Convert the following hexadecimal numbers to decimal:

- (a) FF
- (b) F0A2
- (c) 0F100
- (d) 100

1.25 Convert the following hexadecimal numbers to decimal:

- (a) 10
- (b) 4E3
- (c) FF0
- (d) 200

1.26 Convert the decimal number 128 to the following number systems:

- (a) binary
- (b) hexadecimal
- (c) base three
- (d) base five
- (e) base fifteen

1.27 Compare the number of digits necessary to represent the following decimal numbers in binary, octal, decimal, and hexadecimal representations. You need not determine the actual representations—just the number of required digits. For example, representing the decimal number 12 requires four digits in binary (1100 is the actual representation), two digits in octal (14), two digits in decimal (12), and one digit in hexadecimal (C).

- (a) 8
- (b) 60
- (c) 300
- (d) 1000
- (e) 999,999

1.28 Determine the decimal number ranges that can be represented in binary, octal, decimal, and hexadecimal using the following numbers of digits. For example, 2 digits can represent decimal number range 0 through 3 in binary (00 through 11), 0 through 63 in octal (00 through 77), 0 through 99 in decimal (00 through 99), and 0 through 255 in hexadecimal (00 through FF).

- (a) 1
- (b) 3
- (c) 6
- (d) 8

*image
not
available*

*image
not
available*

*image
not
available*

*image
not
available*


*image
not
available*

► **HOW TRANSISTORS ARE MADE SO SMALL—USING PHOTOGRAPHIC METHODS**

If you took a pencil and made the smallest dot that you could on a sheet of paper, that dot's area would hold many thousands of transistors on a modern silicon chip. How can chip makers create such tiny transistors? The key lies in photographic methods. Chip makers lay a special chemical onto the chip—special because the chemical changes when exposed to light. Chip makers then shine light through a lens that focuses the light down to extremely small regions on the chip—similar to how a microscope's lens lets us see tiny things by focusing light, but in reverse. The chemical in the small illuminated region changes, and then a solvent washes away the chemical—but some regions stay because of the light that changed that region. Those remaining

regions form parts of transistors. Repeating this process over and over again, with different chemicals at different steps, results not only in transistors, but also wires connecting the transistors, and insulators preventing crossing wires from touching.

 Photograph of a Pentium processor's silicon chip, having millions of transistors. Actual size is about 1 cm each side.



Atom or Celeron processor, requires only about 50 million transistors, and the processor in a cell phone, like an ARM processor, may have only a few million transistors. Many of today's high-end chips, like chips inside Internet routers, contain tens or hundreds of such microprocessors, and can conceivably contain thousands of even smaller microprocessors (or just a few very big microprocessors).

IC density has been doubling roughly every 18 months since the 1960s. The doubling of IC density every 18 months is widely known as **Moore's Law**, named after Gordon Moore, a co-founder of Intel Corporation, who made predictions back in 1965 that the number of components per IC would double every year or so. At some point, chip makers won't be able to shrink transistors any further. After all, the transistor has to at least be wide enough to let electrons pass through. People have been predicting the end of Moore's Law for two decades now, but transistors keep shrinking, though in 2009 many observers noted a slowdown.

Not only do smaller transistors and wires provide for more functionality in a chip, but they also provide for faster circuits, in part because electrons need not travel as far to get from one transistor to the next. This increased speed is the main reason why personal computer clock speeds have improved so drastically over the past few decades, from kilohertz frequencies in the 1970s to gigahertz frequencies in the 2000s.

► **2.3 THE CMOS TRANSISTOR**

The most popular type of IC transistor is the CMOS transistor. A detailed explanation of how a CMOS transistor works is beyond the scope of this book, but nevertheless a simplified explanation may satisfy much curiosity.

A chip is made primarily from the element silicon. A chip, also known as an integrated circuit, or IC, is typically about the size of a fingernail. Even if you open up a computer or other chip-based device, you would not actually see the silicon chip, since chips are actually inside a larger, usually black, protective package. But you certainly

*image
not
available*

*image
not
available*

*image
not
available*

44 ► 2 Combinational Logic Design

" $ab=01$ " is shorthand for " $a=0, b=1$."

- OR returns 1 if *either or both* of its operands are 1. So the result of $a \text{ OR } b$ is 1 in any of the following cases: $ab=01$, $ab=10$, $ab=11$. Thus, the only time $a \text{ OR } b$ is 0 is when $ab=00$.
- NOT returns 1 if its operand is 0. So $\text{NOT}(a)$ returns 1 if a is 0, and returns 0 if a is 1.

We use Boolean logic operators frequently in everyday thought, such as in the statement "I'll go to lunch if Mary goes OR John goes, AND Sally does not go." To represent this using Boolean concepts, let F represent my going to lunch ($F=1$ means I'll go to lunch, $F=0$ means I won't go). Let Boolean variables m , j , and s represent Mary, John, and Sally each going to lunch (so $s=1$ would represent Sally going to lunch, else $s=0$). Then we can translate the above English sentence into the Boolean equation:

$$F = (m \text{ OR } j) \text{ AND NOT}(s)$$

So F will equal 1 if either m or j is 1, and s is 0. Now that we've translated the English sentence into a Boolean equation, we can perform several mathematical activities with that equation. One thing we can do is determine the value of F for different values of m , j , and s :

- $m=1, j=0, s=1 \rightarrow F = (1 \text{ OR } 0) \text{ AND NOT}(1) = 1 \text{ AND } 0 = 0$
- $m=1, j=1, s=0 \rightarrow F = (1 \text{ OR } 1) \text{ AND NOT}(0) = 1 \text{ AND } 1 = 1$

In the first case, I don't go to lunch; in the second, I do.

A second thing we could do is apply some algebraic rules (discussed later) to modify the original equation to the equivalent equation:

$$F = (m \text{ and NOT}(s)) \text{ OR } (j \text{ and NOT}(s))$$

In other words, I'll go to lunch if Mary goes AND Sally does not go, OR if John goes AND Sally does not go. That statement, as different as it may look from the earlier statement, is nevertheless equivalent to the earlier statement.

A third thing we could do is formally prove properties about the equation. For example, we could prove that if Sally goes to lunch ($s=1$), then I don't go to lunch ($F=0$) no matter who else goes, using the equation:

$$F = (m \text{ OR } j) \text{ AND NOT}(1) = (m \text{ OR } j) \text{ AND } 0 = 0$$

No matter what the values of m and j , F will equal 0.

Noting all the mathematical activities we can do using Boolean equations, you can start to see what Boole was trying to accomplish in formalizing human reasoning.

Example 2.1 Converting a problem statement to a Boolean equation

Convert the following problem statements to Boolean equations using AND, OR, and NOT operators. F should equal 1 only if:

1. a is 1 and b is 1. Answer: $F = a \text{ AND } b$
2. either of a or b is 1. Answer: $F = a \text{ OR } b$

*image
not
available*

*image
not
available*

*image
not
available*

*image
not
available*

*image
not
available*

*image
not
available*

52 ► 2 Combinational Logic Design

Example 2.8 Seat belt warning light with initial illumination

Let's further extend the previous example. Automobiles typically light up all their warning lights when you first turn the key, so that you can check that all the warning lights are working. Assume that the system receives an input t that is 1 for the first 5 seconds after a key is inserted into the ignition, and 0 afterward (don't worry about who or what sets t in that way). So the system should set $w=1$ when $p=1$ and $s=0$ and $k=1$, OR when $t=1$. Note that when $t=1$, the circuit should illuminate the light, regardless of the values of p , s , and k . The new circuit equation is:

$$w = (p \text{ AND NOT}(s) \text{ AND } k) \text{ OR } t$$

The circuit is shown in Figure 2.25.

 


Figure 2.25 Extended seat belt warning circuit.

Some circuit drawing rules and conventions

There are some rules and conventions that designers commonly follow when drawing circuits of logic gates, as shown in Figure 2.26.

- Logic gates have one or more inputs and one output, but each input and output is typically not labeled. Remember: the order of the inputs into a gate doesn't affect the gate's logical behavior.
- Each wire has an implicit direction, from one gate's output to another gate's input, but we typically don't draw arrows showing each direction.
- A single wire can be branched out into two (or more) wires going to multiple gate inputs—the branches have the same value as the single wire. But two wires can NOT be merged into one wire—what would be the value of that one wire if the incoming two wires had different values?

 


Figure 2.26 Circuit drawing rules.

► 2.5 BOOLEAN ALGEBRA

Logic gates are useful for implementing circuits, but equations are better for manipulating circuits. The algebraic tools of Boolean algebra enable us to manipulate Boolean equations so we can do things like simplify the equations, check whether two equations are equivalent, find the inverse of an equation, prove properties about the equations, etc. Since a Boolean equation consisting of AND, OR, and NOT operations can be straightforwardly transformed into a circuit of AND, OR, and NOT gates, manipulating Boolean equations can be considered as manipulating digital circuits. We'll informally introduce some of the most useful algebraic tools of Boolean algebra. Appendix A provides a formal definition of Boolean algebra.

*image
not
available*

*image
not
available*

*image
not
available*

56 ► 2 Combinational Logic Design

- **Identity**

$$\begin{aligned}0 + a &= a + 0 = a \\1 * a &= a * 1 = a\end{aligned}$$

This one should be intuitive. ORing a with 0 ($a+0$) just means that the result will be whatever a is. After all, $1+0$ is 1, while $0+0$ is 0. Likewise, ANDing a with 1 ($a*1$) results in a . $1*1$ is 1, while $0*1$ is 0.

- **Complement**

$$\begin{aligned}a + a' &= 1 \\a * a' &= 0\end{aligned}$$

This also makes intuitive sense. Regardless of the value of a , a' is the opposite, so you get a 0 and a 1, or you get a 1 and a 0. One of (a, a') will always be a 1, so ORing them ($a+a'$) must yield a 1. Likewise, one of (a, a') will always be a 0, so ANDing them ($a*a'$) must yield a 0.

The following examples apply these basic properties to some digital design examples to see how the properties can help.

Example 2.11 Applying the basic properties of Boolean algebra

Use the properties of Boolean algebra for the following problems:

- Show that abc' is equivalent to $c'ba$.
The commutative property allows swapping the operands being ANDed, so $a*b*c' = a*c'*b = c'*a*b = c'*b*a = c'ba$.
- Show that $abc + abc' = ab$.
The first distributive property allows factoring out the ab term: $abc + abc' = ab(c+c')$. Then, the complement property allows replacing the $c+c'$ by 1: $ab(c+c') = ab(1)$. Finally, the identity property allows removal of the 1 from the AND term: $ab(1) = ab*1 = ab$.
- Show that the equation $x + x'z$ is equivalent to $x + z$.
The second distributive property (the tricky one) allows replacing $x+x'z$ by $(x+x')*(x+z)$. The complement property allows replacing $(x+x')$ by 1, and the identity property allows replacing $1*(x+z)$ by $x+z$.
- Show that $(a+a')bc$ is just bc .
The complement property states that $(a+a')$ is 1, yielding $1*bc$. The identity property then results in bc .
- Multiply out $(w + x)(y + z)$ into sum-of-products form.
First writing $(w + x)$ as A will make clear that the distributive property can be applied: $A(y+z)$. The first distributive property yields $Ay + Az$. Expanding A back yields $(w+x)y + (w+x)z$. Applying the first distributive property again yields $wy + xy + wz + xz$, which is in sum-of-products form.

*image
not
available*

*image
not
available*

*image
not
available*

*image
not
available*

*image
not
available*

*image
not
available*

64 ► 2 Combinational Logic Design

output for every possible input. Thus, notice that truth tables were used in Figure 2.8 to describe in an intuitive manner the behavior of basic logic gates.

A drawback of truth tables is that for a large number of inputs, the number of truth table rows can be very large. Given a function with n inputs, the number of input combinations is 2^n . A function with 10 inputs would have $2^{10} = 1024$ possible input combinations—you can't easily see much of anything in a table having 1024 rows. A function with 16 inputs would have 65,536 rows in its truth table.

Example 2.18 Capturing a function as a truth table

TABLE 2.2 Truth table for 5-or-greater function.

a	b	c	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Create a truth table describing a function that detects whether a three-bit inputs' value, representing a binary number, is 5 or greater. Table 2.2 shows a truth table for the function. We first list all possible combinations of the three input bits, which we've labeled a, b, and c. We then enter a 1 in the output row if the inputs represent 5, 6, or 7 in binary, meaning the last three rows. We enter 0s in all the other rows.

Converting among Boolean Function Representations

Given the above representations, converting from one representation to another is sometimes necessary or useful. For the three representations discussed so far (equations, circuits, and truth tables), there are six possible conversions from one representation to another, as shown in Figure 2.36, which will now be described.

1. Equations to Circuits

Converting an equation to a circuit can be done straightforwardly by using an AND gate for every AND operator, an OR gate for every OR operator, and a NOT gate for every NOT operator. Several examples of such conversions appear in Section 2.4.

2. Circuits to Equations

Converting a circuit into an equation can be done by starting from the circuit's inputs, and then writing the output of each gate as an expression involving the gate's inputs. The expression of the last gate before the output represents the expression for the circuit's function.

 


Figure 2.36 Possible conversions from one Boolean function representation to another.

*image
not
available*

*image
not
available*

*image
not
available*

68 ► 2 Combinational Logic Design

Inputs						Outputs
a	b	c	ab	(ab)'	c'	F
0	0	0	0	1	1	1
0	0	1	0	1	0	0
0	1	0	0	1	1	1
0	1	1	0	1	0	0
1	0	0	0	1	1	1
1	0	1	0	1	0	0
1	1	0	1	0	1	0
1	1	1	1	0	0	0

Figure 2.42 Truth table for the circuit's equation.

From the Boolean equation, we can now construct the truth table for the combinational circuit. Since our circuit has three inputs— a , b , and c —there are $2^3 = 8$ possible combinations of inputs (i.e., $abc = 000, 001, 010, 011, 100, 101, 110, 111$), so the truth table has the eight rows shown in Figure 2.42. For each input, we compute the value of F and fill in the corresponding entry in the truth table. For example, when $a=0$, $b=0$, and $c=0$, F is $(00)' * 0' = (0)' * 1 = 1 * 1 = 1$. We compute the circuit's output for the remaining combinations of inputs using a truth table with intermediate values, shown in Figure 2.42.

Standard Representation and Canonical Form

Standard Representation—Truth Tables

As stated earlier, although there are many equation representations and circuit representations of a Boolean function, there is only one possible truth table representation of a Boolean function. Truth tables therefore represent a *standard representation* of a function—for any function, there may be many possible equations, and many possible circuits, but there is only *one* truth table. The truth table representation is unique.

One use of a standard representation of a Boolean function is for comparing two functions to see if they are equivalent. Suppose you wanted to check whether two Boolean equations represented the same function. One way would be to try to manipulate one equation to be the same as the other equation, like we did in the automatic sliding door example of Example 2.13. But suppose we were not successful in getting them to be the same—is that because they really are not the same, or because we just didn't manipulate the equation enough? How do we really know the two equations do not represent the same function?

A conclusive way to check whether two items represent the same function is to create a truth table for each, and then check whether the truth tables are identical. So to determine whether $F = ab + a'$ is equivalent to $F = a'b' + a'b + ab$, we could generate truth tables for each, using the method described earlier of evaluating the function for each output row, as Figure 2.43.

$F = ab + a'$			$F = a'b' + a'b + ab$		
a	b	F	a	b	F
0	0	1	0	0	1
0	1	1	0	1	1
1	0	0	1	0	0
1	1	1	1	1	1

Figure 2.43 Truth tables showing equivalence.

*image
not
available*

*image
not
available*

*image
not
available*

Example 2.23 Binary number to seven-segment display converter

Many electronic appliances display a number for us to read. Example appliances include a clock, a microwave oven, and a telephone answering machine. A popular and simple device for displaying a single digit number is a *seven-segment display*, illustrated in Figure 2.46.

 


Figure 2.46 Seven-segment display: (a) connections of inputs to segments, (b) input values for numbers 0, 1, and 2, and (c) a pair of real seven-segment display components.

The display consists of seven light segments, each of which can be illuminated independently of the others. A desired digit can be displayed by setting the signals a, b, c, d, e, f, and g appropriately. So to display the digit 8, all seven signals must be set to 1. To display the digit 1, b and c are each set to 1. A few letters can be displayed too, like a lower case “b.”

Commonly, a microprocessor outputs a 4-bit binary number intended to be shown on a seven-segment display as a decimal (base ten) digit. Outputting four rather than seven signals conserves scarce pins on the microprocessor. Thus, a useful combinational circuit converts four bits w, x, y, and z of a binary number to the seven-segment display signals a–g, as in Figure 2.47.

 


Figure 2.47 Binary to seven-segment converter.

The desired circuit behavior is easily captured as a table, shown in Table 2.4. In case the microprocessor outputs a number greater than 9, no segments are activated.

We can create a custom logic circuit to implement the converter. Note that Table 2.4 is in the form of a truth table having multiple outputs (a through g). We can treat each output separately, designing a circuit for a, then for b, etc. Summing the terms corresponding to the 1s in the a column (as was done in Figure 2.40) leads to the following equation for a:

$$a = w'x'y'z' + w'x'yz' + w'x'yz + w'xy'z + w'xyz' + w'xyz + wx'y'z' + wx'y'z$$

Likewise, summing the terms for the 1s in the b column leads to the following equation for b:

$$b = w'x'y'z' + w'x'y'z + w'x'yz' + w'x'yz + w'xy'z' + w'xyz + wx'y'z' + wx'y'z$$

Equations could similarly be created for the remaining outputs c through g. Finally, a circuit could be created for a having 8 4-input AND gates and an 8-input OR gate, another circuit for b having 8 4-input AND gates and an 8-input OR gate, and so on for c through g. We could, of course, have minimized the logic for each equation before creating each of the circuits.

You may notice that the equations for a and b have several terms in common. For example, the term $w'x'y'z'$ appears in both equations. So it would make sense for both outputs to share one

For this example, starting from a truth table is a more natural choice than an equation.

*image
not
available*

*image
not
available*

*image
not
available*

Step 2A: Create equations. We create equations (as was done in Figure 2.40) for each output as follows:

$$y = a'bc + ab'c + abc' + abc$$

$$z = a'b'c + a'bc' + ab'c' + abc$$

We can simplify the first equation algebraically:

$$y = a'bc + ab'c + ab(c' + c) = a'bc + ab'c + ab$$

Step 2B: Implement as a gate-based circuit. We then create the final circuits for the two outputs, as shown in Figure 2.49.

 


Figure 2.49 Number-of-1s counter gate-based circuit.

Simplifying Circuit Notations

Some new simplifying notations were used in the circuits in the previous example. One simplifying notation is to list the inputs multiple times, as in Figure 2.50(a). Such listing reduces lines in a drawing crossing one another. An input listed multiple times is assumed to have been branched from the same input.

 


Figure 2.50 Simplifying circuit notations: (a) listing inputs multiple times to reduce drawing of crossing wires, (b) using inversion bubbles or complemented input to reduce NOT gates drawn.

Another simplifying notation is the use of an inversion bubble at the input of a gate, rather than the use of an inverter, as in Figure 2.50(b). An *inversion bubble* is a small circle drawn at the input of a gate as shown, indicating that the signal is inverted. An external input that has inversion bubbles at many gates is assumed to feed through a single inverter that is then branched out to those gates. An alternative simplification is to simply list the input as complemented, like b' shown in the figure.

 
 
*image
not
available*

*image
not
available*

*image
not
available*

► 2.8 MORE GATES

Designers use several other types of gates beyond just AND, OR, and NOT. Those gates include NAND, NOR, XOR, and XNOR.

NAND & NOR

A **NAND** gate (short for “not AND”) has the opposite output of an AND gate, outputting a 0 only when all inputs are 1, and outputting a 1 otherwise (meaning at least one input is 0). A NAND gate has the same behavior as an AND gate followed by a NOT gate. Figure 2.54(a) illustrates a NAND gate.

A **NOR** gate (“not OR”) has the opposite output as an OR gate, outputting a 0 if at least one input is 1, and outputting 1 if all inputs are 0. A NOR gate has the same behavior as an OR gate followed by a NOT gate. Figure 2.54(b) shows a NOR gate.

Whereas Boolean algebra has the symbols “*” and “+” for the AND and OR operations, no such commonly-used operator symbols exist for NAND and NOR. Instead, the NAND operation on variables a and b would be written as $(a * b)'$ or just $(ab)'$, and the NOR operation would be written as $(a + b)'$.

 


Figure 2.54 Additional gates: (a) NAND, (b) NOR, (c) XOR, (d) XNOR.

Section 2.4 warned that the shown CMOS transistor implementations of AND and OR gates were not realistic. The reason is because pMOS transistors don't conduct 0s very well, but they conduct 1s just fine. Likewise, nMOS transistors don't conduct 1s well, but they conduct 0s just fine. The reasons for these asymmetries are beyond this book's scope. The implications are that the AND and OR gates in Figure 2.8 are not feasible, as they rely on pMOS transistors to conduct 0s (but pMOS conducts 0s poorly) and nMOS transistors to conduct 1s (but nMOS conducts 1s poorly). However, if we switch the locations of power and ground in the AND and OR circuits of Figure 2.8, the results are the NAND and NOR gate circuits shown in Figure 2.54(a) and Figure 2.54(b).

*image
not
available*

*image
not
available*

*image
not
available*

84 ► 2 Combinational Logic Design

N -variable function will have 2^N rows in its truth table. Then, note that each row can output one of two possible values. Thus, the number of possible functions will be $2 * 2 * 2 * \dots 2^N$ times. Therefore, the total number of functions is:

$$2^{2^N}$$

So there are: $2^{2^3} = 2^8 = 256$ possible Boolean functions of 3 variables, and $2^{2^4} = 2^{16} = 65536$ possible functions of 4 variables.

► 2.9 DECODERS AND MUXES

Two additional components, a decoder and a multiplexer, are also commonly used as digital circuit building blocks, though they themselves can be built from logic gates.

Decoders

A decoder is a higher-level building block commonly used in digital circuits. A **decoder** decodes an input n -bit binary number by setting exactly one of the decoder's 2^n outputs to 1. For example, a 2-input decoder, illustrated in Figure 2.62(a), would have $2^2 = 4$ outputs, d_3, d_2, d_1, d_0 . If the two inputs $i_1 i_0$ are 00, d_0 would be 1 and the remaining outputs would be 0. If $i_1 i_0 = 01$, d_1 would be 1. If $i_1 i_0 = 10$, d_2 would be 1. If $i_1 i_0 = 11$, d_3 would be 1. One and only one output of a decoder will ever be 1 at a given time, corresponding to the particular current value of the inputs, as shown in Figure 2.62(a).

The internal design of a decoder is straightforward. Consider a 2x4 decoder. Each output d_0, d_1, d_2 , and d_3 is a distinct function. d_0 should be 1 only when $i_1=0$ and $i_0=0$, so $d_0 = i_1' i_0'$. Likewise, $d_1 = i_1' i_0$, $d_2 = i_1 i_0'$, and $d_3 = i_1 i_0$. Thus, we build the decoder with one AND gate for each output, connecting the true or complemented values of i_1 and i_0 to each gate, as shown in Figure 2.62.

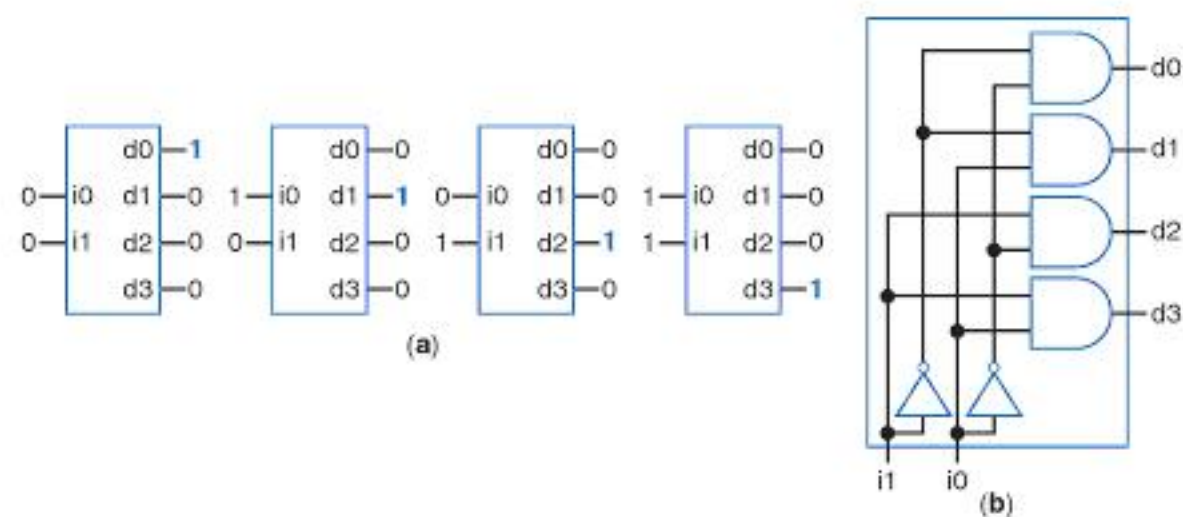


Figure 2.62 2x4 decoder: (a) outputs for possible input combinations, (b) internal design.

*image
not
available*

*image
not
available*

*image
not
available*

*image
not
available*

*image
not
available*

*image
not
available*

94 ► 2 Combinational Logic Design


likely to be correct. However, sometimes designers start with an equation rather than a truth table, as in Example 2.24. A designer can reverse engineer the circuit to an equation, but that equation may be different than the original equation, especially if the designer algebraically manipulated the original equation when designing the circuit. Furthermore, checking that two equations are equivalent may require converting to canonical form (sum-of-minterms), which may result in huge equations if the function has a large number of inputs.

In fact, even if a designer didn't make any mistakes in converting a mental understanding of the desired function into a truth table or equation, how does the designer know that the original understanding was correct?

A commonly used method for checking that a circuit works as expected is called simulation. **Simulation** of a circuit is the process of providing sample inputs to the circuit and running a computer program that computes the circuit's output for the given inputs. A designer can then check that the output matches what is expected. The computer program that performs simulation is called a **simulator**.

To use simulation to check a circuit, a designer must describe the circuit using a method that enables computer programs to read the circuit. One method of describing a circuit is to draw the circuit using a schematic capture tool. A **schematic capture tool**

Figure 2.75 Display snapshot of a commercial schematic capture tool.

 

allows a user to place logic gates on a computer screen and to draw wires connecting those gates. The tool allows users to save their circuit drawings as computer files. All the circuit drawings in this chapter have represented examples of schematics—for example, the circuit drawing in Figure 2.62(b), which showed a 2x4 decoder, was an example of a schematic. Figure 2.75 shows a schematic for the same design, drawn using a popular commercial schematic capture tool. Schematic capture is used not only to capture circuits for simulator tools, but also for tools that map our circuits to physical implementations, which will be discussed in Chapter 7.

Once a designer has created a circuit using schematic capture, the designer must provide the simulator with a set of inputs that will be used to check for proper output. One way of providing the inputs is by drawing waveforms for the circuit's inputs. An input's **waveform** is a line that goes from left to right, representing the value of the input as time proceeds to the right. The line is drawn high to represent 1 and low to represent 0

*image
not
available*

*image
not
available*



*image
not
available*

- 2.24 For the function $F = a'd' + a'c + b'cd' + cd$:
- List all the variables.
 - List all the literals.
 - List all the product terms.
- 2.25 Let variables T represent being tall, H being heavy, and F being fast. Let's consider anyone who is not tall as short, not heavy as light, and not fast as slow. Write a Boolean equation to represent each of the following:
- You may ride a particular amusement park ride only if you are either tall and light, or short and heavy.
 - You may NOT ride an amusement park ride if you are either tall and light, or short and heavy. Use algebra to simplify the equation to sum of products.
 - You are eligible to play on a particular basketball team if you are tall and fast, or tall and slow. Simplify this equation.
 - You are NOT eligible to play on a particular football team if you are short and slow, or if you are light. Simplify to sum-of-products form.
 - You are eligible to play on both the basketball and football teams above, based on the above criteria. Hint: combine the two equations into one equation by ANDing them.
- 2.26 Let variables S represent a package being small, H being heavy, and E being expensive. Let's consider a package that is not small as big, not heavy as light, and not expensive as inexpensive. Write a Boolean equation to represent each of the following:
- Your company specializes in delivering packages that are both small and inexpensive (a package must be small AND inexpensive for us to deliver it); you'll also deliver packages that are big but only if they are expensive.
 - A particular truck can be loaded with packages only if the packages are small and light, small and heavy, or big and light. Simplify the equation.
 - Your above-mentioned company buys the above-mentioned truck. Write an equation that describes the packages your company can deliver. Hint: Appropriately combine the equations from the above two parts.
- 2.27 Use algebraic manipulation to convert the following equation to sum-of-products form:
 $F = a(b + c)(d') + ac'(b + d)$
- 2.28 Use algebraic manipulation to convert the following equation to sum-of-products form:
 $F = a'b(c + d') + a(b' + c) + a(b + d)c$
- 2.29 Use DeMorgan's Law to find the inverse of the following equation: $F = abc + a'b$. Reduce to sum-of-products form. Hint: Start with $F' = (abc + a'b)'$
- 2.30 Use DeMorgan's Law to find the inverse of the following equation: $F = ac' + abd' + acd$. Reduce to sum-of-products form.

SECTION 2.6: REPRESENTATIONS OF BOOLEAN FUNCTIONS

- 2.31 Convert the following Boolean equations to a digital circuit:
- $F(a, b, c) = a'bc + ab$
 - $F(a, b, c) = a'b$
 - $F(a, b, c) = abc + ab + a + b + c$
 - $F(a, b, c) = c'$

100 ► 2 Combinational Logic Design

  
Figure 2.78 Combinational circuit for F .

Figure 2.79 Combinational circuit for G .

- 2.32 Create a Boolean equation representation of the digital circuit in Figure 2.78.
- 2.33 Create a Boolean equation representation for the digital circuit in Figure 2.79.
- 2.34 Convert each of the Boolean equations in Exercise 2.31 to a truth table.
- 2.35 Convert each of the following Boolean equations to a truth table:
- $F(a, b, c) = a' + bc'$
 - $F(a, b, c) = (ab)' + ac' + bc$
 - $F(a, b, c) = ab + ac + ab'c' + c'$
 - $F(a, b, c, d) = a'bc + d'$

TABLE 2.9 Truth table.

a	b	c	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

TABLE 2.10 Truth table.

a	b	c	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

TABLE 2.11 Truth table.

 
 
a	b	c	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

TABLE 2.8 Truth table.


Inputs		Output		
a	b	ab	b'	ab+b'
0	0			
0	1			
1	0			
1	1			

- 2.36 Fill in Table 2.8's columns for the equation: $F = ab + b'$
- 2.37 Convert the function F shown in the truth table in Table 2.9 to an equation. Don't minimize the equation.
- 2.38 Use algebraic manipulation to minimize the equation obtained in Exercise 2.37.
- 2.39 Convert the function F shown in the truth table in Table 2.10 to an equation. Don't minimize the equation.
- 2.40 Use algebraic manipulation to minimize the equation obtained in Exercise 2.39.
- 2.41 Convert the function F shown in the truth table in Table 2.11 to an equation. Don't minimize the equation.
- 2.42 Use algebraic manipulation to minimize the equation obtained in Exercise 2.41.
- 2.43 Create a truth table for the circuit of Figure 2.78.
- 2.44 Create a truth table for the circuit of Figure 2.79.
- 2.45 Convert the function F shown in the truth table in Table 2.9 to a digital circuit.
- 2.46 Convert the function F shown in the truth table in Table 2.10 to a digital circuit.
- 2.47 Convert the function F shown in the truth table in Table 2.11 to a digital circuit.
- 2.48 Convert the following Boolean equations to canonical sum-of-minterms form:
- $F(a, b, c) = a'bc + ab$
 - $F(a, b, c) = a'b$
 - $F(a, b, c) = abc + ab + a + b + c$
 - $F(a, b, c) = c'$

- 2.49 Determine whether the Boolean functions $F = (a + b)' * a$ and $G = a + b'$ are equivalent, using (a) algebraic manipulation and (b) truth tables.
- 2.50 Determine whether the Boolean functions $F = ab'$ and $G = (a' + ab)'$ are equivalent, using (a) algebraic manipulation and (b) truth tables.
- 2.51 Determine whether the Boolean function $G = a'b'c + ab'c + abc' + abc$ is equivalent to the function represented by the circuit in Figure 2.80.
- 2.52 Determine whether the two circuits in Figure 2.81 are equivalent circuits, using (a) algebraic manipulation and (b) truth tables.

Figure 2.80 Combinational circuit for H .Figure 2.81 Combinational circuits for F and G .

- 2.53 * Figure 2.82 shows two circuits whose inputs are unlabeled.
- (a) Determine whether the two circuits are equivalent. Hint: Try all possible labelings of the inputs for both circuits.
- (b) How many circuit comparisons would need to be performed to determine whether two circuits with 10 unlabeled inputs are equivalent?

 Figure 2.82 Combinational circuits for F and G .

SECTION 2.7: COMBINATIONAL LOGIC DESIGN PROCESS

- 2.54 A museum has three rooms, each with a motion sensor (m_0 , m_1 , and m_2) that outputs 1 when motion is detected. At night, the only person in the museum is one security guard who walks from room to room. Create a circuit that sounds an alarm (by setting an output A to 1) if motion is ever detected in more than one room at a time (i.e., in two or three rooms), meaning there must be one or more intruders in the museum. Start with a truth table.
- 2.55 Create a circuit for the museum of Exercise 2.54 that detects whether the guard is properly patrolling the museum, detected by *exactly* one motion sensor being 1. (If no motion sensor is 1, the guard may be sitting, sleeping, or absent.)

102 ► 2 Combinational Logic Design

- 2.56 Consider the museum security alarm function of Exercise 2.54, but for a museum with 10 rooms. A truth table is not a good starting point (too many rows), nor is an equation describing when the alarm should sound (too many terms). However, the inverse of the alarm function can be straightforwardly captured as an equation. Design the circuit for the 10-room security system by designing the inverse of the function, and then just adding an inverter before the circuit's output.
- 2.57 A network router connects multiple computers together and allows them to send messages to each other. If two or more computers send messages simultaneously, the messages "collide" and must be re-sent. Using the combinational design process of Table 2.5, create a collision detection circuit for a router that connects 4 computers. The circuit has 4 inputs labeled M0 through M3 that are 1 when the corresponding computer is sending a message and 0 otherwise. The circuit has one output labeled C that is 1 when a collision is detected and 0 otherwise.
- 2.58 Using the combinational design process of Table 2.5, create a 4-bit prime number detector. The circuit has four inputs—N3, N2, N1, and N0—that correspond to a 4-bit number (N3 is the most significant bit) and one output P that is 1 when the input is a prime number and that is 0 otherwise.
- 2.59 A car has a fuel-level detector that outputs the current fuel-level as a 3-bit binary number, with 000 meaning empty and 111 meaning full. Create a circuit that illuminates a "low fuel" indicator light (by setting an output L to 1) when the fuel level drops below level 3.
- 2.60 A car has a low-tire-pressure sensor that outputs the current tire pressure as a 5-bit binary number. Create a circuit that illuminates a "low tire pressure" indicator light (by setting an output T to 1) when the tire pressure drops below 16. Hint: you might find it easier to create a circuit that detects the inverse function. You can then just append an inverter to the output of that circuit.

SECTION 2.8: MORE GATES

- 2.61 Show the conduction paths and output value of the NAND gate transistor circuit in Figure 2.54 when: (a) $x = 1$ and $y = 0$, (b) $x = 1$ and $y = 1$.
- 2.62 Show the conduction paths and output value of the NOR gate transistor circuit in Figure 2.54 when: (a) $x = 1$ and $y = 0$, (b) $x = 0$ and $y = 0$.
- 2.63 Show the conduction paths and output value of the AND gate transistor circuit in Figure 2.55 when: (a) $x = 1$ and $y = 1$, (b) $x = 0$ and $y = 1$.
- 2.64 Two people, denoted using variables A and B, want to ride with you on your motorcycle. Write a Boolean equation that indicates that exactly one of the two people can come ($A=1$ means A can come; $A=0$ means A can't come). Then use XOR to simplify your equation.
- 2.65 Simplify the following equation by using XOR wherever possible: $F = a'b + ab' + cd' + c'd + ac$.
- 2.66 Use 2-input XOR gates to create a circuit that outputs a 1 when the number of 1s on inputs a, b, c, d is odd.
- 2.67 Use 2-input XOR or XNOR gates to create a circuit that detects whether an even number of the inputs a, b, c, d are 1s.

SECTION 2.9: DECODERS AND MUXES

- 2.68 Design a 3x8 decoder using AND, OR, and NOT gates.
- 2.69 Design a 4x16 decoder using AND, OR, and NOT gates.
- 2.70 Design a 3x8 decoder with enable using AND, OR, and NOT gates.
- 2.71 Design an 8x1 multiplexer using AND, OR, and NOT gates.

- 2.72 Design a 16x1 multiplexer using AND, OR, and NOT gates.
- 2.73 Design a 4-bit 4x1 multiplexer using four 4x1 multiplexers.
- 2.74 A house has four external doors, each with a sensor that outputs 1 if its door is open. Inside the house is a single LED that a homeowner wishes to use to indicate whether a door is open or closed. Because the LED can only show the status of one sensor, the homeowner buys a switch that can be set to 0, 1, 2, or 3 and that has a 2-bit output representing the switch position in binary. Create a circuit to connect the four sensors, the switch, and the LED. Use at least one mux (a single mux or an N -bit mux) or decoder. Use block symbols, each with a clearly defined function, such as “2x1 mux,” “8-bit 2x1 mux,” or “3x8 decoder”; do not show the internal design of a mux or decoder.
- 2.75 A video system can accept video from one of two video sources, but can only display one source at a given time. Each source outputs a stream of digitized video on its own 8-bit output. A switch with a single-bit output chooses which of the two 8-bit streams will be passed on a display’s single 8-bit input. Create a circuit to connect the two video sources, the switch, and the display. Use at least one mux (a single mux or an N -bit mux) or decoder. Use block symbols, each with a clearly defined function, such as “2x1 mux,” “8-bit 2x1 mux,” or “3x8 decoder”; do not show the internal design of a mux or decoder.
- 2.76 A store owner wishes to be able to indicate to customers that the items in one of the store’s eight aisles are temporarily discounted (“on sale”). The store owner thus mounts a light above each aisle, and each light has a single-bit input that turns on the light when 1. The store owner has a switch that can be set to 0, 1, 2, 3, 4, 5, 6, or 7, and that has a 3-bit output representing the switch position in binary. A second switch can be set up or down and has a single-bit output that is 1 when the switch is up; the store owner can set this switch down if no aisles are currently discounted. Use at least one mux (a single mux or an N -bit mux) or decoder. Use block symbols, each with a clearly defined function, such as “2x1 mux,” “8-bit 2x1 mux,” or “3x8 decoder”; do not show the internal design of a mux or decoder.

SECTION 2.10: ADDITIONAL CONSIDERATIONS

- 2.77 Determine the critical path of the following specified circuits. Assume that each AND and OR gate has a delay of 1 ns, each NOT gate has a delay of 0.75 ns, and each wire has a delay of 0.5 ns.
- (a) The circuit of Figure 2.37.
 - (b) The circuit of Figure 2.41.
- 2.78 Design a 1x4 demultiplexer using AND, OR, and NOT gates.
- 2.79 Design an 8x3 encoder using AND, OR, and NOT gates. Assume that only one input will be 1 at any given time.
- 2.80 Design a 4x2 priority encoder using AND, OR, and NOT gates. If every input is 0, the encoder output should be 00.

► **DESIGNER PROFILE**

Samson enjoyed physics and math in college, and focused his advanced studies on integrated circuit (IC) design, believing the industry to have a great future. Years later, he realizes his belief was true: “Looking back 20 years in high tech, we have experienced four major revolutions: the PC

revolution, digital revolution, communication revolution, and Internet revolution—all four enabled by the IC industry. The impact of these revolutions to our daily life is profound.”

He has found his job to be “very challenging, interesting, and exciting. I continually learn new skills to keep up, and to do my job more efficiently.”

One of Samson’s key design projects was for digital television, namely, high-definition TV (HDTV), involving companies like Zenith, Philips, and Intel. In particular, he led the 12-person design team that built Intel’s first liquid crystal on silicon (LCoS) chip for rear-projection HDTV. “Traditional LCoS chips are analog. They apply different analog voltages on each pixel of the display chip so it can produce an image. But analog LCoS is very sensitive to noise and temperature variation. We used digital signals to do pulse width modulation on each pixel.” Samson is quite proud of his team’s accomplishments: “Our HDTV picture quality was much better.”

Samson also worked on the 200-member design team for Intel’s Pentium II processor. That was a very different

experience. “For the smaller team project, each person had more responsibility, and overall efficiency was high. For the large team project, each person worked on a specific part of the project—the chip was divided into clusters, each cluster into units, and each unit had a leader. We relied heavily on design flows and methodologies.”

Samson has seen the industry’s peaks and valleys during the past two decades: “Like any industry, the IC job market has its ups and downs.” He believes the industry survives the low points in large part due to innovation. “Brand names sell products, but without innovation, markets go elsewhere. So we have to be very innovative, creating new products so that we are always ahead in the global competition.”

But “innovation doesn’t grow on trees,” Samson points out. “There are two kinds of innovations. The first is invention, which requires a good understanding of the physics behind technology. For example, to make an analog TV into a digital TV, we must know how human eyes perceive video images, which parts can be digitized, how digital images can be produced on a silicon chip, etc. The second kind of innovation reuses existing technology for a new application. For example, we can reuse advanced space technologies in a new non-space product serving a bigger market. e-Bay is another example—it reused Internet technology for online auctions. Innovations lead to new products, and thus new jobs for many years.”

Thus, Samson points out that “The industry is counting on new engineers from college to be innovative, so they can continue to drive the high-tech industry forward. When you graduate from college, it’s up to *you* to make things better.”

Sequential Logic Design: Controllers

▶ 3.1 INTRODUCTION

The output of a combinational circuit is a function of the circuit's present inputs. A combinational circuit has no *memory*—the feature of a circuit storing new bits and retaining those bits over time for later use. Combinational circuits alone are of limited usefulness. Designers typically use combinational circuits as part of larger circuits called sequential circuits—circuits that have memory. A *sequential circuit* is a circuit whose output depends not only on the circuit's present inputs, but also on the circuit's present *state*, which is all the bits currently stored in the circuit. The circuit's state in turn depends on the past *sequence* of the circuit's input values.

An everyday sequential system example is a lamp that toggles (changes from off to on, or from on to off) when its button is pressed, as was shown in Figure 2.1(c). After plugging in the lamp, push the lamp's button (the input) a first time, and the lamp turns on. Push the button a second time, and the lamp turns off. Push the button a third time, and the lamp turns on again. The system's output (whether the lamp is on or off) depends on the input and on whether the system is currently in the *state* of the lamp being on or off. That state in turn depends on the past sequence of input values since the system was initially powered on. In contrast, an everyday combinational system example is a basic doorbell, as was shown in Figure 2.1(a). Push the button (the input) now, and the bell (the output) rings. Push the button again, and the bell rings again. Push the button tomorrow and the bell rings the same each time. A basic doorbell has no state—its output value (whether the bell rings or not) depends solely on its present input value (whether the button is pressed or not).

Most digital systems with which you are likely familiar involve sequential circuits. A calculator contains a sequential circuit to store the numbers you enter, in order to operate on those numbers. A digital camera stores pictures. A traffic light controller stores information indicating which light is presently green. A kitchen timer that counts down from a set time to zero stores the present count value, to know what the next value should be.

This chapter describes sequential circuit building blocks called flips-flops and registers, which can store bits. It then introduces a sequential circuit design process in which a designer first captures desired behavior, and then converts that behavior to a type of sequential circuit known as a controller, comprised of a register and combinational logic.

► 3.2 STORING ONE BIT—FLIP-FLOPS

Sequential circuit design is aided by a building block that enables storing of a bit, much like combinational circuit design was aided by the AND, OR, and NOT gate building blocks. Storing a bit means that we can save either a 0 or a 1 in the block and later come back to see what was saved. For example, consider designing the flight attendant call-button system in Figure 3.1. An airline passenger can push the *Call* button to turn on a small blue light above the passenger's seat, indicating to a flight attendant that the passenger needs service. The light stays on even after the call button is released. The light can be turned off by pressing the *Cancel* button. Because the light must stay on even after the call button is released, a mechanism is needed to “remember” that the call button was pressed. That mechanism can be a bit storage block, in which a 1 will be stored when the call button is pressed, and a 0 stored when the cancel button is pressed. The inputs of this bit storage block will be connected to the call and cancel buttons, and the output to the blue light, as in Figure 3.1. The light illuminates when the block's output is 1.

This section introduces the internal design of such a bit storage block by introducing several increasingly complex circuits able to store a bit—a basic SR latch, a level-sensitive SR latch, a level-sensitive D latch, and an edge-triggered D flip-flop. The D flip-flop will then be used to create a block capable of storing multiple bits, known as a register, which will serve as the main bit storage block in the rest of the book. Each successive circuit eliminates some problem of the previous one. Be aware that designers today rarely use bit storage blocks other than D flip-flops. We introduce the other blocks to provide the reader with an underlying intuition of the D flip-flop's internal design.

 


Figure 3.1 Flight attendant call-button system. Pressing *Call* turns on the light, which stays on after *Call* is released. Pressing *Cancel* turns off the light.

Feedback—The Basic Storage Method

The basic method used to store a bit in a digital circuit is *feedback*. You've surely experienced feedback in the form of audio feedback, when someone talking into a microphone stood in front of the speaker, causing a loud continuous humming sound to come out of the speakers (in turn causing everyone to cover their ears and snicker). The talker generated a sound that was picked up by the microphone, came out of the speakers (amplified), was picked up *again* by the microphone, came out the speakers again (amplified even more), etc. That's feedback.

Feedback in audio systems is annoying, but in digital systems is extremely useful. Intuitively, we know that somehow the output of a logic gate must feed back into the gate itself, so that the stored bit ends up looping around and around, like a dog chasing its own tail. We might try the circuit in Figure 3.2.

Suppose initially Q is 0 and S is 0. At some point, suppose we set S to 1. That causes Q to become 1, and that 1 feeds back into the OR gate, causing Q to be 1, etc. So even when S returns

 


Figure 3.2 First (failed) attempt at using feedback to store a bit.

 


Figure 3.3 Tracing the behavior of our first attempt at bit storage.

to 0, Q stays 1. Unfortunately, Q stays 1 from then on, and we have no way of resetting Q to 0. But hopefully you understand the basic idea of feedback now—we did successfully store a 1 using feedback, but we couldn't store a 0 again.

Figure 3.3 shows the timing diagram for the feedback circuit of Figure 3.2. Initially, we set both OR gate inputs to 0 (Figure 3.3(a)). Then we set S to 1 (Figure 3.3(b)), which causes Q to become 1 slightly later (Figure 3.3(c)), assuming the OR gate has a small delay as discussed in Section 2.10. Q becoming 1 causes t to become 1 slightly later (Figure 3.3(d)), assuming the wire has a small delay too. Q will stay at 1. Finally, when we change S back to 0 (Figure 3.3(e)), Q will continue to stay 1 because t is 1. The first curved line with an arrow indicates that the event of S changing from 0 to 1 causes the event of Q changing from 0 to 1. An **event** is any change on a bit signal from 0 to 1 or from 1 to 0. The second curved line with an arrow indicates that the event of Q changing from 0 to 1 in turn causes the event of t changing from 0 to 1. That 1 then continues to loop around, forever, with no way for S to reset Q to 0.

Basic SR Latch

It turns out that the simple circuit in Figure 3.4, called a **basic SR latch**, implements the bit storage building block that we seek. The circuit consists of a pair of cross-coupled NOR gates. Making the circuit's S input equal to 1 causes Q to become 1, while making R equal to 1 causes Q to become 0. Making both S and R equal to 0 causes Q 's current value to keep looping around. In other words, S “sets” the latch to 1, and R “resets” the latch to 0—hence the letters S (for *set*) and R (for *reset*).

Let's see why the basic SR latch works as it does. Recall that a NOR gate outputs 1 only when all the gate's inputs equal 0, as shown in Figure 3.5; if at least one input equals 1, the NOR gate outputs 0.

 


Figure 3.5 NOR behavior.

 





Figure 3.4 Basic SR latch.

108 ► 3 Sequential Logic Design: Controllers

Suppose we make $S=0$ and $R=1$, as in the SR latch circuit of Figure 3.6, and that the values of Q and t are initially unknown. Because the bottom gate of the circuit has at least one input equal to 1 (R), the gate outputs 0—in the timing diagram, R becoming 1 causes Q to become 0. In the circuit, Q 's 0 feeds back to the top NOR gate, which will have both its inputs equal to 0, and thus its output will be 1. In the timing diagram, Q becoming 0 causes t to become 1. In the circuit, that 1 feeds back to the bottom NOR gate, which has at least one input (actually, both) equal to 1, so the bottom gate continues to output 0. Thus the output Q equals 0, and all values are *stable*, meaning the values won't change as long as no external input changes.

Now suppose we keep $S=0$ and change R from 1 back to 0, as in Figure 3.7. The bottom gate still has at least one input equal to 1 (the input coming from the top gate), so the bottom gate continues to output 0. The top gate continues to have both inputs equal to 0 and continues to output 1. The output Q will thus still be 0. Therefore, the earlier $R=1$ stored a 0 into the SR latch, also known as *resetting* the latch, and that 0 remains stored even when R is changed back to 0. Note that $R=1$ will reset the latch regardless of the initial value of Q .

Consider making $S=1$ and $R=0$, as in Figure 3.8. The top gate in the circuit now has one input equal to 1, so the top gate outputs a 0—the timing diagram shows the change of S from 0 to 1, causing t to change from 1 to 0. The top gate's 0 output feeds back to the bottom gate, which now has both inputs equal to 0 and thus outputs 1—the timing diagram shows the change of t from 1 to 0, causing Q to change from 0 to 1. The bottom gate's 1 output (Q) feeds back to the top gate, which has at least one input (actually, both of its inputs) equal to 1, so the top gate continues to output 0. The output Q therefore equals 1, and all values are stable.

   Figure 3.6 SR latch when $S=0$ and $R=1$.Figure 3.7 SR latch when $S=0$ and $R=0$, after R was previously 1.Figure 3.8 SR latch when $S=1$ and $R=0$.

Next, consider making $S=0$ and $R=0$ again, as in Figure 3.9. The top gate still has at least one input equal to 1 (the input coming from the bottom gate), so the top gate continues to output 0. The bottom gate continues to have both inputs equal to 0 and continues to output 1. The output Q is still 1. Thus, the earlier $S=1$ stored a 1 into the SR latch, also known as *setting* the latch, and that 1 remains stored even when we return S to 0. Note that $S=1$ will set the latch regardless of the initial value of Q .

 


Figure 3.9 SR latch when $S=0$ and $R=0$, after S was previously 1.

 


Figure 3.10 Flight attendant call-button system using a basic SR latch.

The basic SR latch can be used to implement the flight attendant call-button system as shown in Figure 3.10, by connecting the call button to S , the cancel button to R , and Q to the light. Pressing the call button sets Q to 1, thus turning on the light. Q stays 1 even when the call button is released. Pressing the cancel button resets Q to 0, thus turning off the light. Q stays 0 even when the cancel button is released.

Problem when $SR=11$ in a Basic SR latch

A problem with the basic SR latch is that if S and R are both 1, undefined behavior results—the latch might store a 1, it might store a 0, or its output might oscillate, changing from 1 to 0 to 1 to 0, and so on. In particular, if $S=1$ and $R=1$ (written as “ $SR=11$ ” for short), both the NOR gates have at least one input equal to 1, and thus both gates output 0, as in Figure 3.11(a). A problem occurs when S and R are made 0 again. Suppose S and R return to 0 at the same time. Then both gates will have 0s at all their inputs, so each gate’s output will change from 0 to 1, as in Figure 3.11(b). Those 1s feed back to the gates’ inputs, causing the gates to output 0s, as in Figure 3.11(c). Those 0s feed back to the gate inputs again, causing the gates to output 1s. And so on. Going from 1 to 0 to 1 to 0 repeatedly is called *oscillation*. Oscillation is not a desirable feature of a bit storage block.

 


Figure 3.11 The situation of $S=1$ and $R=1$ causes problems— Q oscillates when SR return to 00.

110 ► 3 Sequential Logic Design: Controllers

In a real circuit, the delays of the upper and lower gates and wires would be slightly different from one another. So after some time of oscillation, one of the gates will get ahead of the other, outputting a 1 before the other does, then a 0 before the other does, until it gets far enough ahead to cause the circuit to enter a stable situation of either $Q=0$ or $Q=1$. Which situation will happen is unknown beforehand. A situation in which the final output of a sequential circuit depends on the delays of gates and wires is a **race condition**. Figure 3.12 shows a race condition involving oscillation but ending with a stable situation of $Q=1$.

 


Figure 3.12 Q eventually settles to either 0 or 1, due to race condition.

 


Figure 3.13 Circuit added external to SR latch striving to prevent $SR=11$ when both buttons are pressed.

Therefore, S and R must *never* be allowed to simultaneously equal 1 in an SR latch. A designer using an SR latch should add a circuit external to the SR latch that strives to ensure that S and R never simultaneously equal 1. For example, in the flight attendant call-button system of Figure 3.10, a passenger pushing both buttons at the same time might result in oscillation in the SR latch and hence a blinking light. The SR latch will eventually settle to 1 or 0, and thus the light will end up either on or off. A designer might therefore decide that if both buttons are pressed then the call button should take priority so that SR won't both be 1. Such behavior can be achieved using a combinational circuit in

front of S and R , as shown in Figure 3.13. S should be 1 if the call button (denoted as $Call$) is pressed and either the cancel button ($Cncl$) is pressed or not pressed, so $S = Call * Cncl + Call * Cncl' = Call$. R should be 1 only if the cancel button is pressed *and* the call button is *not* pressed, meaning $R = Cncl * Call'$. The circuit in Figure 3.13 is derived directly from these equations.

Even with such an external circuit, S and R could still inadvertently both become 1 due to the delay of real gates (see Section 2.10). Assume the AND and NOT gates in Figure 3.13 have delays of 1 ns each (ignore wire delays for now). Suppose the cancel button is being pressed and hence $SR=01$, as in Figure 3.14, and then the call button is also pressed. S will change from 0 to 1 almost immediately, but R will remain at 1 for 2 ns longer, due to the AND and NOT gate delays, before changing to 0. SR would therefore be 11 for 2 ns. A temporary unintended signal value caused by circuit delays is called a **glitch**.

 


Figure 3.14 Gate delays can cause $SR=11$.

Significantly, glitches can also cause an unintended latch set or reset. Assume that the wire connecting the cancel button to the AND gate in Figure 3.13 has a delay of 4 ns (perhaps the wire is very long), in addition to the 1 ns AND and NOT gate delays. Suppose both buttons are pressed, so $SR=10$, and then the buttons are both released— SR should become 00 . S will indeed change to 0 almost immediately. The top input of the AND gate will become 1 after the 1 ns delay of the NOT gate. The bottom input of that AND gate will remain 1 for 3 ns more, due to the 4 ns wire delay, thus causing R to change 1. After that bottom input finally changes to 0, yet another 1 ns will pass due to the AND gate delay before R returns to 0. Thus, R experienced a 4 ns glitch, which resets the latch to 0—yet a reset is clearly not what the designer intended.

 


Figure 3.15 Wire delay leading to a glitch causing a reset.

Level-Sensitive SR Latch

A partial solution to the glitch problem is to extend the SR latch to have an *enable* input C as in Figure 3.16. When $C=1$, the S and R signals pass through the two AND gates to the $S1$ and $R1$ inputs of the basic SR latch, because $S*1=S$ and $R*1=R$. The latch is enabled. But when $C=0$, the two AND gates cause $S1$ and $R1$ to be 0, regardless of the values of S and R . The latch is disabled. The enable input can be set to 0 when S and R might change so that glitches won't propagate through to $S1$ and $R1$, and then set to 1 only when S and R are stable. The question then remains of when to set the enable input to 1. That question will be answered in the upcoming sections.

 


Figure 3.16 Level-sensitive SR latch—an SR latch with enable input C .

Figure 3.17 shows the call button system from Figure 3.13, this time using an SR latch with an enable input C . The timing diagram shows that if $Cncl$ is 1 and then $Call$ is changed to 1, a glitch of $SR=11$ occurs, as was already shown in Figure 3.14. However, because $C=0$, $S1R1$ stay at 00 . When we later set the enable input to 1, the stable SR values propagate through to $S1R1$. An SR latch with an enable is called a **level-sensitive SR latch**, because the latch is only sensitive to its S and R inputs when the level of the enable input is 1. It is also called a **transparent SR latch**, because setting the enable input to 1 makes the internal SR latch transparent to the S and R inputs. It is also sometimes called a **gated SR latch**.

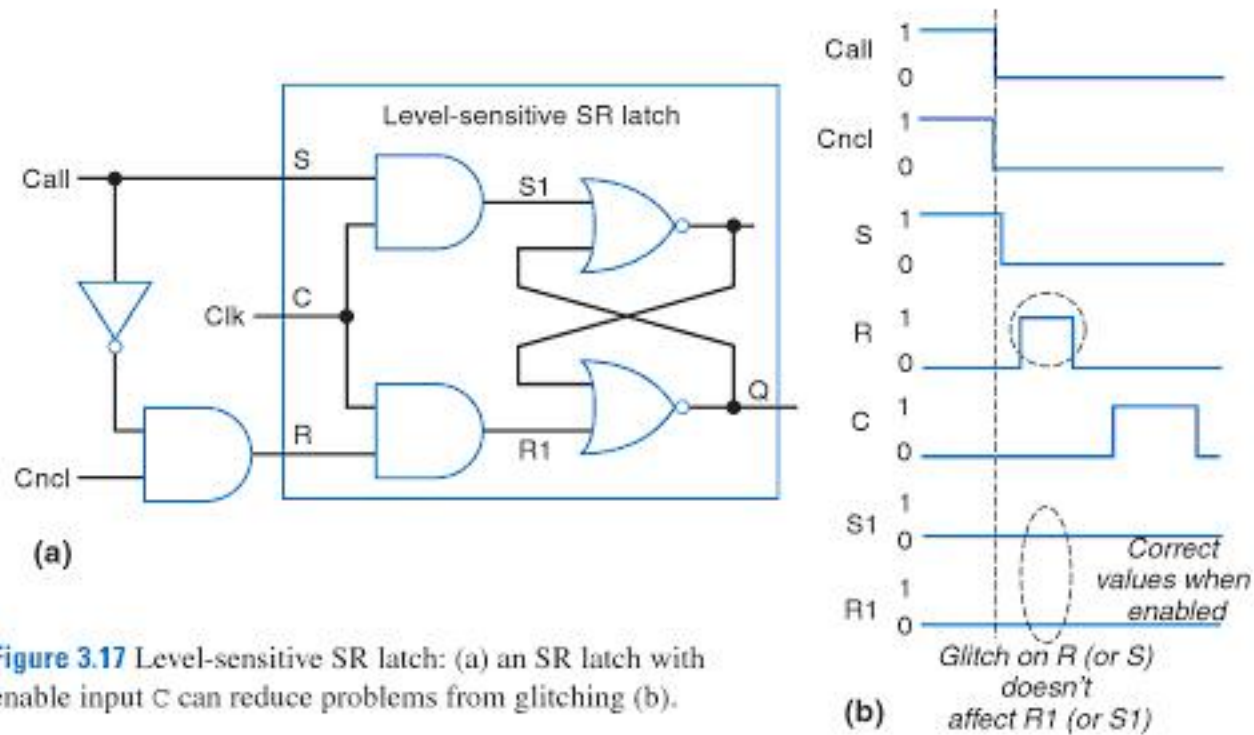


Figure 3.17 Level-sensitive SR latch: (a) an SR latch with enable input C can reduce problems from glitching (b).

Notice that the top NOR gate of an SR latch outputs the opposite value as the bottom NOR gate that outputs Q. Thus, an output Q' can be included on an SR latch almost for free, just by connecting the top gate to an output named Q' . Most latches come with both Q and Q' outputs. The symbol for a level-sensitive SR latch with such dual outputs is shown in Figure 3.18.

 


Figure 3.18 Symbol for dual-output level-sensitive SR latch.

Level-Sensitive D Latch—A Basic Bit Store

A designer using a level-sensitive SR latch has the burden of ensuring that S and R are never simultaneously 1 when the enable input is 1. One way to relieve designers of this burden is to introduce another type of latch, called a *level-sensitive D latch* (also known as a *transparent D latch* or *gated D latch*), shown in Figure 3.19. Internally, the latch's D input connects directly to the S input of a level-sensitive SR latch, and connects through an inverter to the R input of the SR latch. The D latch is thus either setting (when $D=1$) or resetting (when $D=0$) its internal basic SR latch when the enable input C is 1.

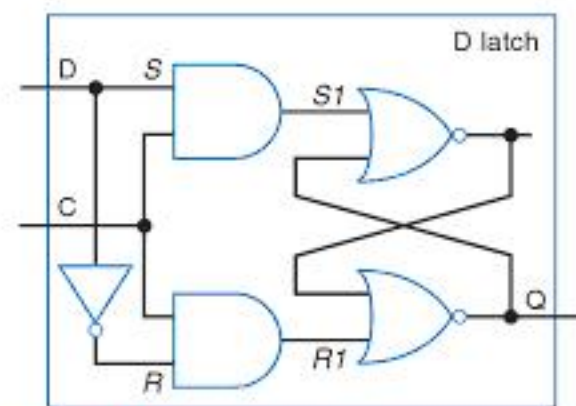


Figure 3.19 D latch internal circuit.

A level-sensitive D latch thus stores whatever value is present at the latch's D input when $C = 1$, and remembers that value when $C = 0$. Figure 3.20 shows a timing diagram of a D latch for sample input values on D and C; arrows indicate which signal changes cause other signals to change. When D is 1 and C is 1, the latch is set to 1, because S1 is 1 and R1 is 0. When D is 0 and C is 1, the latch is reset to 0, because R1 is 1 and S1 is 0. By making R the opposite of S, the D latch ensures that S and R won't both be 1 at the same time, as long as D is only changed when C is 0 (even if changed when C is 1, the inverter's delay could cause S and R to both be 1 briefly, but for too short of time to cause a problem).

The symbol for a D latch with dual-outputs (Q and Q') is shown in Figure 3.21.

 


Figure 3.20 D latch timing diagram.

 


Figure 3.21 D latch symbol.

Edge-Triggered D Flip-Flop—A Robust Bit Store

The D latch still has a problem that can cause unpredictable circuit behavior—namely, signals can propagate from a latch output to another latch's input while the clock signal is 1. For example, consider the circuit in Figure 3.22 and the pulsing enable signals—a **pulse** is a change from 0 to 1 and back to 0, and a pulsing enable signal is called a **clock** signal. When $Clk = 1$, the value on Y will be loaded into the first latch and appear at that latch's output. If Clk still equals 1, then that value will also get loaded into the second latch. The value will keep propagating through the latches until Clk returns to 0. Through how many latches will the value propagate for a pulse on Clk ? It's hard to say—we would have to know the precise timing delay information of each latch.

Figure 3.22 A problem with latches—through how many latches will Y propagate for each pulse of Clk_A ? For Clk_B ?

 


Figure 3.23 illustrates this propagation problem in more detail. Suppose D1 is initially 0 for a long time, changes to 1 long enough to be stable, and then Clk becomes 1. $Q1$ will thus change from 0 to 1 after about three gate delays, and thus D2 will also change from 0 to 1, as shown in the left timing diagram. If Clk is still 1, then that new value for D2 will propagate through the AND gates of the second latch, causing S2 to change from 0 to 1 and R2 from 1 to 0, thus changing $Q2$ from 0 to 1, as shown in the left timing diagram.

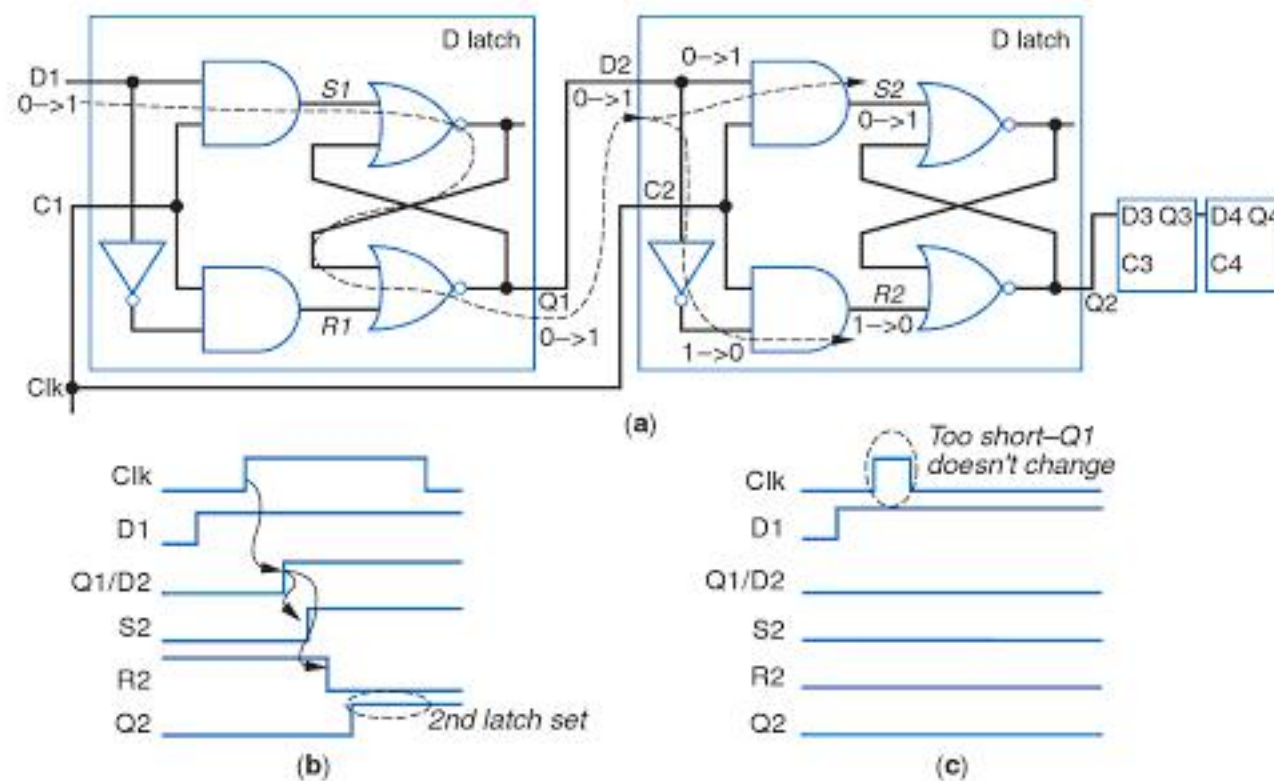


Figure 3.23 A problem with level-sensitive latches: (a) while $C = 1$, $Q1$'s new value may propagate to $D2$, (b) such propagation can cause an unknown number of latches along a chain to get updated, (c) trying to shorten the clock's time at 1 to avoid propagation to the next latch, but long enough to allow a latch to reach a stable feedback situation, is hard because making the clock's high time too short prevents proper loading of the latch.

You might suggest making the clock signal such that the clock is 1 only for a short amount of time, so there's not enough time for the new output of a latch to propagate to the next latch's inputs. But how short is short enough? 50 ns? 10 ns? 1 ns? 0.1 ns? And if we make the clock's time at 1 too short, that time may not be long enough for the bit at a latch's D input to stabilize in the latch's feedback circuit, and we might therefore not successfully store the bit, as illustrated in Figure 3.23(c).

A good solution is to design a more robust block for storing a bit—a block that stores the bit at the D input at the *instant* that the clock rises from 0 to 1. Note that we didn't say that the block stores the bit instantly. Rather, the bit that will eventually get stored into the block is the bit that was stable at D at the instant that the clock rises from 0 to 1. Such a block is called an **edge-triggered**

D flip-flop. The word “edge” refers to the vertical part of the line representing the clock signal, when the signal transitions from 0 to 1. Figure 3.24 shows three cycles of a clock signal, and indicates the three rising clock edges of those cycles.



Figure 3.24 Rising clock edges.

Edge-Triggered D Flip-Flop Using a Master-Servant Design. One way to design an edge-triggered D flip-flop is to use *two* D latches, as shown in Figure 3.25.

The first D latch, known as the **master**, is enabled (can store new values on D_m) when Clk is 0 (due to the inverter), while the second D latch, known as the **servant**, is enabled

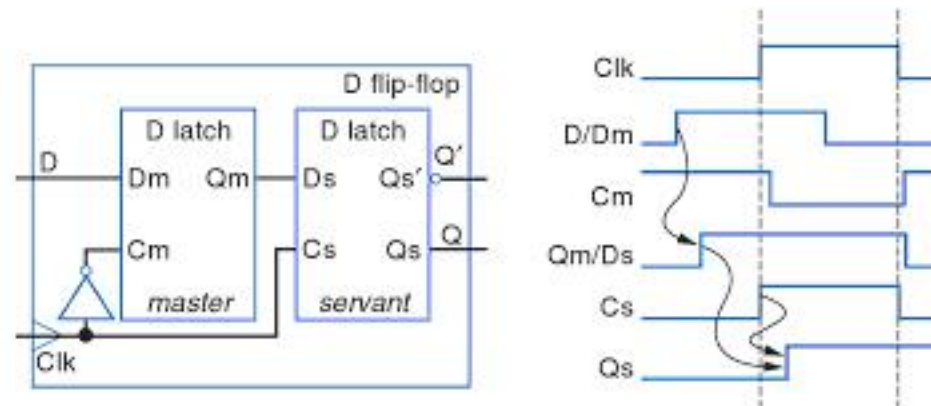


Figure 3.25 A D flip-flop implementing an edge-triggered bit storage block, internally using two D latches in a master-servant arrangement. The master D latch stores its D_m input while $Clk = 0$, but the new value appearing at Q_m , and hence at D_s , does not get stored into the servant latch, because the servant latch is disabled when $Clk = 0$. When Clk becomes 1, the servant D latch becomes enabled and thus gets loaded with whatever value was in the master latch at the instant that Clk changed from 0 to 1.

when Clk is 1. Thus, while Clk is 0, the bit on D is stored into the master latch, and hence Q_m and D_s are updated—but the servant latch does not store this new bit, because the servant latch is not enabled since Clk is not 1. When Clk becomes 1, the master latch becomes disabled, thus holding whatever bit was at the D input just before the clock changed from 0 to 1. Also, when Clk is 1, the servant latch becomes enabled, thus storing the bit that the master is storing, and that bit is the bit that was at the D input just before Clk changed from 0 to 1. The two latches thus implement an edge-triggered storage block—the bit that was at the input when Clk changed from 0 to 1 gets stored.

The edge-triggered block using two internal latches thus prevents the stored bit from propagating through more than one flip-flop when the clock is 1. Consider the chain of flip-flops in Figure 3.26, which is similar to the chain in Figure 3.22 but with D flip-flops in place of D latches.

 


Figure 3.26 Using D flip-flops, we now know through how many flip-flops Y will propagate for Clk_A and for Clk_B —one flip-flop exactly per pulse, for either clock signal.

We know that Y will propagate through exactly one flip-flop on each clock cycle.

The drawback of a master-servant approach is that two D latches are needed to store one bit. Figure 3.26 shows four flip-flops, but there are two latches inside each flip-flop, for a total of eight latches.

Many alternative methods exist other than the master-servant method for designing an edge-triggered flip-flop. In fact, there are hundreds of different designs for latches and flip-flops beyond the designs shown above, with those designs differing in terms of their size, speed, power, etc. When using an edge-triggered flip-flop, a designer usually doesn't consider whether the flip-flop achieves edge-triggering using the master-servant method or using some other method. The designer need only know that the flip-flop is edge-triggered.

The common name is actually "master-slave." Some choose instead to use the term "servant," due to many people finding the term "slave" offensive. Others use the terms "primary-secondary."

gered, meaning the data value present when the clock edge is rising is the value that gets loaded into the flip-flop and that will appear at the flip-flop's output some time later.

The above discussion is for what is known as **positive** or **rising** edge-triggered flip-flops, which are triggered by the clock signal changing from 0 to 1. There are also flip-flops known as **negative** or **falling** edge-triggered flip-flops, which are triggered by the clock changing from 1 to 0. A negative edge-triggered D flip-flop can be built using a master-servant design where the second flip-flop's clock input is inverted, rather than the first flip-flop's.

Positive edge-triggered flip-flops are drawn using a small triangle at the clock input, and negative edge-triggered flip-flops are drawn using a small triangle along with an inversion bubble, as shown in Figure 3.27. Because those symbols identify the clock input, those inputs typically are not given a name.

Bear in mind that although the master-servant design doesn't change the output until the falling clock edge, the flip-flop is still positive edge-triggered, because the flip-flop stored the value that was at the D input at the instant that the clock edge was *rising*.

 


Figure 3.27 Positive (shown on the left) and negative (right) edge-triggered D flip-flops. The sideways triangle input represents an edge-triggered clock input.

Latches versus Flip-Flops: Various textbooks define the terms latch and flip-flop differently. We'll use what seems to be the most common convention among designers, namely:

- A **latch** is level-sensitive, and
- A **flip-flop** is edge-triggered.

So saying "edge-triggered flip-flop" would be redundant, since flip-flops are, by this definition, edge-triggered. Likewise, saying "level-sensitive latch" is redundant, since latches are by definition level-sensitive.

Figure 3.28 uses a timing diagram to illustrate the difference between level-sensitive (latch) and edge-triggered (flip-flop) bit storage blocks. The figure provides an example of a clock signal and a value on a signal D. The next signal trace is for the Q output of a D latch, which is level-sensitive. The latch ignores the first pulse on D (labeled as 3 in the figure) because Clk is low. However, when Clk becomes high (1), the latch output follows the D input, so when D changes from 0 to 1 (4), so does the latch output (7). The latch ignores the next changes on D when Clk is low (5), but then follows D again when Clk is high (6, 8).

 


Figure 3.28 Latch versus flip-flop timing.

Designers commonly refer to flip-flops as just "flops."

The circuit's desired behavior can be captured as the truth table in Table 3.1. If $Call=0$ and $Cncl=0$ (the first two rows), D equals Q 's value. If $Call=0$ and $Cncl=1$ (the next two rows), $D=0$. If $Call=1$ and $Cncl=0$ (the next two rows), $D=1$. And if both $Call=1$ and $Cncl=1$ (the last two rows), the $Call$ button gets priority, so $D=1$.

After some algebraic simplification, we obtain the following equation for D :

$$D = Cncl'Q + Call$$

We can then convert the equation to the circuit shown in Figure 3.34(b). That circuit is more robust than the earlier circuit using an SR latch in Figure 3.10. But it is still not as good as it could be; Section 3.5 will explain why we might want to add additional flip-flops at the $Call$ and $Cncl$ inputs. Furthermore, our design process in this example was ad hoc; the following two sections will introduce better methods for capturing desired behavior and converting to a circuit.

TABLE 3.1 D truth table for call-button system.

Call	Cncl	Q	D
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

The above sections went through several intermediate bit storage block designs before arriving at the robust D flip-flop design. Figure 3.35 summarizes those designs, including features and problems of each. Notice that the D flip-flop relies on an internal SR latch to maintain a stored bit *between* clock edges, and relies on the designer to introduce feedback outside the D flip-flop to maintain a stored bit *across* clock edges.

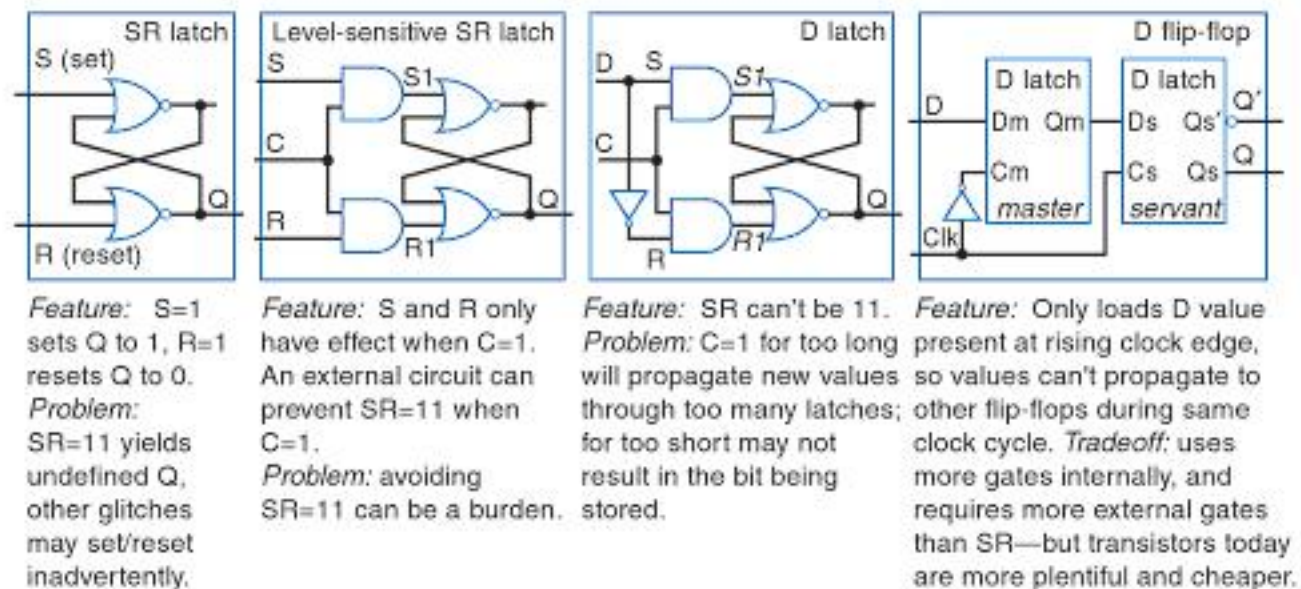


Figure 3.35 Increasingly better bit storage blocks, leading to the D flip-flop.

► A BIT OF HISTORY—RS, JK, T, AND D LATCHES AND FLIP-FLOPS.

Many textbooks, especially those with origins in the 1970s and 1980s, introduce several types of latches and flip-flops and use many pages to describe how to design sequential circuits using those different types. In the 1980s, transistors on ICs were more costly and scarcer than today. The D flip-flop-based design for the call-button system in Figure 3.34(b) uses more transistors than the SR-latch-based design in Figure 3.10—not only does a D flip-flop contain more transistors internally, but it may require more external logic to set D to the appropriate value. Other flip-flop types included a JK flip-flop that acts like an SR flip-flop plus the behavior that the flip-flop toggles if both inputs are 1 (toggle

means to change from 0 to 1, or from 1 to 0), and a T flip-flop with a single input T that toggles the flip-flop when 1. For a given desired behavior, using a particular flip-flop type could save transistors. Designing sequential circuits for any flip-flop type was a challenging task, involving something called “excitation tables” and comparison of different designs, and was helpful for reducing circuit transistors. But today, in the era of billion-transistor ICs, the savings of such flip-flops are trivial. Nearly all modern sequential circuits use D flip-flops and hence are created using the more straightforward design process introduced in this chapter.

Basic Register—Storing Multiple Bits

A **register** is a sequential component that can store multiple bits. A basic register can be built simply by using multiple D flip-flops as shown in Figure 3.36. That register can hold four bits. When the clock rises, all four flip-flops get loaded with inputs I0, I1, I2, and I3 simultaneously.

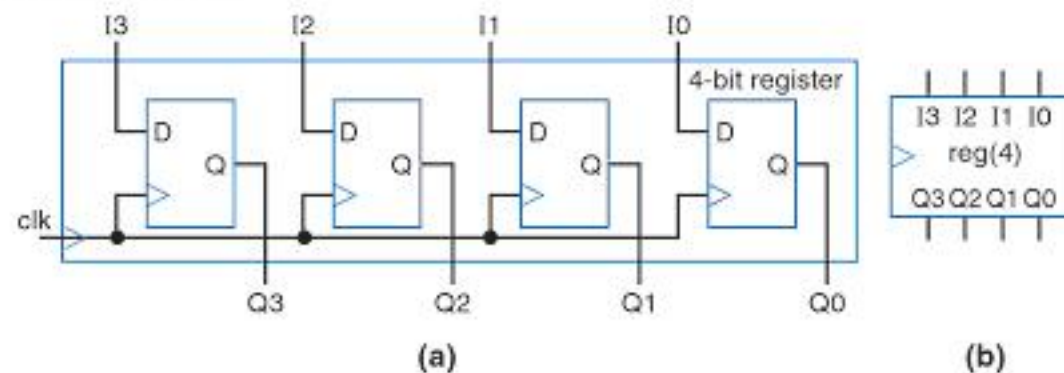


Figure 3.36 A basic 4-bit register: (a) internal design, (b) block symbol.

Such a register, made simply from multiple flip-flops, is the most basic form of a register—so basic that some companies refer to such a register simply as a “4-bit D flip-flop.” Chapter 4 introduces more advanced registers having additional features and operations.

Example 3.2 Temperature history display using registers

We want to design a system that records the outside temperature every hour and displays the last three recorded temperatures, so that an observer can see the temperature trend. An architecture of the system is shown in Figure 3.37.

A timer generates a pulse on signal C every hour. A temperature sensor outputs the present temperature as a 5-bit binary number ranging from 0 to 31, corresponding to those temperatures in Celsius. Three displays convert their 5-bit binary inputs into a numerical display.

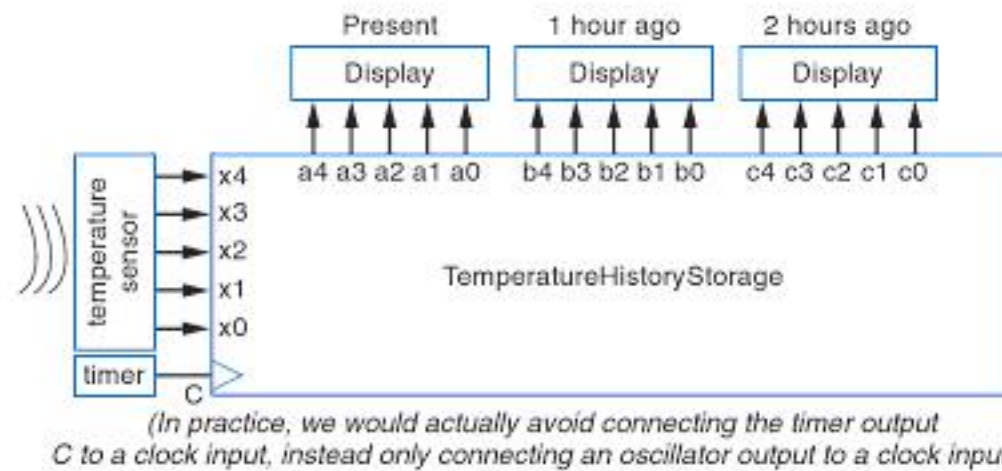


Figure 3.37 Temperature history display system.

We can implement the *TemperatureHistoryStorage* component using three 5-bit registers, as shown in Figure 3.38. Each pulse on signal *C* loads *Ra* with the present temperature on inputs *x4* . . . *x0* (by loading the 5 flip-flops inside *Ra* with the 5 input bits). At the same time that register *Ra* gets loaded with that present temperature, register *Rb* gets loaded with the value that was in *Ra*. Likewise, *Rc* gets loaded with *Rb*'s value. All three loads happen at the same time, namely, on the rising edge of *C*. The effect is that the values that were in *Ra* and *Rb* just before the clock edge are shifted into *Rb* and *Rc*, respectively.


 


Figure 3.38 Internal design of the *TemperatureHistoryStorage* component.

Figure 3.39 shows sample values in the registers for several clock cycles, assuming all the registers initially held 0s, and assuming that as time proceeds the inputs *x4* . . . *x0* have the values shown at the top of the timing diagram.

Figure 3.39 Example of values in the *TemperatureHistoryStorage* registers. One particular data item, 18, is shown moving through the registers on each clock cycle.

 

This example demonstrates one of the desirable aspects of synchronous circuits built from edge-triggered flip-flops—many things happen at once, yet we need not be concerned about signals propagating too fast through a register to another register. The reason we need not be concerned is because registers *only get loaded on the rising clock edge*, which effectively is an infinitely small period of time, so by the time signals propagate through a register to a second register, it's too late—that second register is no longer paying attention to its data inputs.

In practice, designers avoid connecting anything but an oscillator's output to the clock input of a register. A key reason is so that automated tools that analyze a circuit's timing characteristics can work properly; such tools are beyond the scope of this book. We connected a timer's output, which pulsed once per hour, in the above example for the purpose of an intuitive introduction to registers. A better implementation would instead have an oscillator connected to the clock input, and then use the “load” input of a register when the timer output pulsed. The load input of a register will be introduced in Chapter 4.

► 3.3 FINITE-STATE MACHINES (FSMS)

Registers store bits in a digital circuit. Stored bits mean the circuit has **memory** resulting in sequential circuits. A circuit's **state** is the value of all a circuit's stored bits. While a register storing bits happens to result in a circuit with state, state can be intentionally used to design circuits that have a specific behavior over time. For example, we can specifically design a circuit that outputs a 1 for exactly three cycles whenever a button is pressed. We could design a circuit that blinks lights in a specific pattern. We could design a circuit that detects if three buttons get pushed in a particular sequence and then unlocks a door. All these cases make use of state to create specific time-ordered behavior for a circuit.

Example 3.3 Three-cycles-high laser timer—a poorly done first design

Consider the design of a part of a laser surgery system, such as a system for scar removal or corrective vision. Such systems work by turning on a laser for a precise amount of time (see “How does it work?—Laser surgery” on page 123). A general architecture of such a system is shown in Figure 3.40.

A surgeon activates the laser by pressing the button. Assume that the laser should then stay on for exactly 30 ns. Assume that the system's clock period is 10 ns, so that 3 clock cycles last 30 ns. Assume that b from the button is synchronized with the clock and stays high for exactly 1 clock cycle. We need to design a controller component that, once detecting that $b = 1$, holds x high for exactly 3 clock cycles, thus turning on the laser for 30 ns.

This is one example for which a microprocessor solution may not work. Using a microprocessor's programming statements that read input ports and write output ports may not provide a way to hold an output port high for exactly 30 ns—for example, when the microprocessor clock frequency is not fast enough.

 


Figure 3.40 Laser timer system.

Let's try to create a sequential circuit implementation for the system. After thinking about the problem for a while, we might come up with the (bad) implementation in Figure 3.41.

Knowing the output should be held high for three clock cycles, we used three flip-flops, with the idea being that we'll shift a 1 through those three flip-flops, taking three clock cycles for the bit to move through all three flip-flops. We ORed the flip-flop outputs to generate signal x , so that if any flip-flop contains a 1, the laser will be on. We made b the input to the first flip-flop, so when $b=1$, the first flip-flop stores a 1 on the next rising clock edge. One clock cycle later, the second flip-flop will get loaded with 1, and assuming b has now returned to 0, the first flip-flop will get loaded with 0. One clock cycle later, the third flip-flop will get loaded with 1, and the second flip-flop with 0. One clock cycle later, the third flip-flop will get loaded with 0. Thus, the circuit held the output x at 1 for three clock cycles after the button was pressed.

 


Figure 3.41 First (bad) attempt to implement the laser timer system.

We did a poor job implementing this system. First, what happens if the surgeon presses the button a second time before the three cycles are completed? Such a situation could cause the laser to stay on too long. Is there a simple way to fix our circuit to account for that behavior? Second, we didn't use any orderly process for designing the circuit—we came up with the ORing of flip-flop outputs, but how did we come up with that? Will that method work for all time-ordered behavior that needs to be designed?

Two things are required to do a better job at designing circuits having time-ordered behavior: (1) a way to explicitly *capture* the desired time-ordered behavior, and (2) a technique for *converting* such behavior to a sequential circuit.

► HOW DOES IT WORK?—LASER SURGERY.

Laser surgery has become very popular in the past two decades, and has been enabled due to digital systems. Lasers, invented in the early 1960s, generate an intense narrow beam of coherent light, with photons having a single wavelength and being in phase (like being in rhythm) with one another. In contrast, a regular light's photons fly out in all directions, with a diversity of wavelengths. Think of a laser as a platoon of soldiers marching in synch, while a regular light is more like kids running out of school at the end-of-the-day bell. A laser's light can be so intense as to even cut steel. The ability of a digital circuit to carefully control the location, intensity, and duration of the laser is what makes lasers so useful for surgery.

One popular use of lasers for surgery is for scar removal. The laser is focused on the damaged cells slightly below the surface, causing those cells to be vaporized. The laser can also be used to vaporize skin

cells that form bumps on the skin, due to scars or moles. Similarly, lasers can reduce wrinkles by smoothing the skin around the wrinkle to make the crevices more gradual and hence less obvious, or by stimulating tissue under the skin to stimulate new collagen growth.

Another popular use of lasers for surgery is for correcting vision. In one popular laser eye surgery method, the surgeon uses a laser to cut open a flap on the surface of the cornea, and then uses a laser to reshape the cornea by thinning the cornea in a particular pattern, with such thinning accomplished through vaporizing cells.

A digital system controls the laser's location, energy, and duration, based on programmed information of the desired procedure. The availability of lasers, combined with low-cost high-speed digital circuits, makes such precise and useful surgery now possible.

The above examples illustrate that a *finite-state machine* or *FSM* is a mathematical formalism consisting of several items:

- A set of states. The above example had four states: {*On1*, *On2*, *On3*, *Off*}.
- A set of inputs and a set of outputs. The example had one input: {*b*}, and one output: {*x*}.
- An *initial state*: the state in which to start when the system is first powered on. An FSM's initial state can be shown graphically by a directed edge (an edge with an arrow at one end) starting from no state and pointing to the initial state. An FSM can only have one initial state. The example's initial state was the state named *Off*. Note that *Off* is just a name, and does not suggest that the system's power is off (rather, it suggests that the laser is off).
- A set of transitions: An indication of the next state based on the current state and the current values of the inputs. The example used directed edges with associated input *conditions*, which is a Boolean expression of input variables, to indicate the next state. Those edges with conditions are called *transitions*. The example had several transitions, such as the edge with condition $b * clk^{\wedge}$.
- A description of what output values to assign in each state. The example assigns a value to *x* in every state. Assigning an output in an FSM is known as an *action*.

After being defined, an FSM can then be executed (even if just mentally)—what computer programmers might call “running” the FSM. The FSM starts with the current state being the initial state and then transitions to a different state based on the current state and input values, continuing as time proceeds. In each state, the FSM sets output values. Mentally executing an FSM is akin to mentally evaluating a Boolean equation for sample input values.

The FSM in Figure 3.45 would be interpreted as follows. The system starts in the initial state *Off*. The system stays in state *Off* until one of the state's two outgoing transitions has a true condition. One of those transitions has the condition of $b' * clk^{\wedge}$ —in that case, the system transitions right back to state *Off*. The other transition has the condition of $b * clk^{\wedge}$ —in that case, the system transitions to state *On1*. The system stays in state *On1* until its only outgoing transition's condition clk^{\wedge} becomes true—in which case the system transitions to state *On2*. Likewise, the system stays in *On2* until the next rising clock edge, transitioning to *On3*. The system stays in *On3* until the next rising clock edge, transitioning back to state *Off*. State *Off* has associated the action of setting $x=0$, while the states *On1*, *On2*, and *On3* each set $x=1$.

► “STATE” I UNDERSTAND, BUT WHY THE TERMS “FINITE” AND “MACHINE?”

Finite-state machines, or FSMs, have a rather awkward name that sometimes causes confusion. The term “finite” is there to contrast FSMs with a similar representation used in mathematics that can have an infinite number of states; that representation is not very useful in digital design. FSMs, in contrast, have a limited, or finite, number of states. The term

“machine” is used in its mathematical or computer science sense, being a *conceptual* object that can execute an abstract language—specifically, that sense of machine is *not* hardware. Finite-state machines are also known as *finite-state automata*. FSMs are used for many things other than just digital design.

The FSM in Figure 3.45 precisely describes the desired time-ordered behavior of the laser timer system from Example 3.3.

It is interesting to examine the behavior of this FSM if the button is pressed a second time while the laser is on. Notice that the transitions among the *On* states are independent of the value of *b*. So this system will always turn the laser on for exactly three cycles and then return to the *Off* state to await another press of the button.

 


Figure 3.46 Simplifying notation: implicit rising clock edge on every transition.



Figure 3.48 Transition is taken on next rising clock edge.

Simplifying FSM Notation: Making the Rising Clock Implicit

Thus far the rising clock edge (clk^{\wedge}) has appeared in the condition of every FSM transition, because this book only considers the design of sequential circuits that are synchronous and that use rising edge-triggered flip-flops to store bits. Synchronous circuits with edge-triggered flip-flops make up the majority of sequential circuits in modern practice. As such, to make state diagrams more readable, most textbooks and designers follow the convention shown in Figure 3.46 wherein every FSM transition is *implicitly ANDed* with a rising clock edge. For example, a transition labeled “a” actually means “ $a * \text{clk}^{\wedge}$.” Subsequent state diagrams will not include the rising clock edge in transition conditions, instead following the convention that *every* transition is implicitly ANDed with a rising clock edge. Figure 3.47 illustrates the laser timer state diagram from Figure 3.45, redrawn using implicit rising clock edges.

A transition with no associated condition as in Figure 3.48 simply transitions on the next rising clock edge, because of the implicit rising clock edge.

Following are more examples showing how FSMs can describe time-ordered behavior.

Example 3.4 Secure car key

Have you noticed that the keys for many new automobiles have a thicker plastic head than in the past (see Figure 3.49)? The reason is that, believe it or not, there is a computer chip inside the head of the key, implementing a secure car key. In a basic version of such a secure car key, when the driver turns the key in the ignition, the car’s computer (which is under the hood and communicates using what’s called the *basestation*) sends out a radio signal asking the car key’s chip to respond by sending an identifier via a radio signal. The chip in the key then responds by sending the identifier



Figure 3.49 Why are the heads of car keys getting thicker? Note that the key on the right is thicker than the key on the left. The key on the right has a computer chip inside that sends an identifier to the car’s computer, thus helping to reduce car thefts.

 


Figure 3.47 Laser timer state diagram assuming every transition is ANDed with a rising clock.

128 ► 3 Sequential Logic Design: Controllers

(ID), using what's known as a *transponder* (a transponder “transmits” in “response” to a request). If the basestation does not receive a response or the key's response has an ID different than the ID programmed into the car's computer, the computer shuts down and the car won't start.

Let's design the controller for such a key, having an ID of 1011 (real IDs are typically 32 bits long or more, not just 4 bits). Assume the controller has an input a that is 1 when the car's computer requests the key's ID. Thus the controller initially waits for the input a to become 1. The key should then send its ID (1011) serially, starting with the rightmost bit, on an output r ; the key sends 1 on the first clock cycle, 1 on the second cycle, 0 on the third cycle, and finally 1 on the fourth cycle. The FSM for the controller is shown in Figure 3.50. Note that the FSM

sends the bits starting from the bit on the right, which is known as the *least significant bit* (LSB). The computer chip in the car key has circuitry that converts radio signals to bits and vice versa.

Figure 3.51 provides a timing diagram for the FSM for a particular situation. When we set $a = 1$, the FSM enters state $K1$ and outputs $r = 1$. The FSM then proceeds through $K2$, $K3$, and $K4$, outputting $r = 1, 0$, and 1 , respectively, even though we returned input a to 0.

Timing diagrams represent a particular situation defined by how we set the inputs. What would have happened if we had held $a = 1$ for many more clock cycles? The timing diagram in Figure 3.52 illustrates that situation. Notice how in that case the FSM, after returning to state $Wait$, proceeds to state $K1$ again on the next cycle.

“So my car key may someday need its batteries replaced?” you might ask. Actually, no—those chips in keys draw their power, as well as their clock, from the magnetic component of the radio-frequency field generated from the computer basestation, as in RFID chips. The extremely low power requirement makes custom digital circuitry, rather than instructions on a microprocessor, a preferred implementation.

Computer chip keys make stealing cars a lot harder—no more “hot-wiring” to start a car, since the car's computer won't work unless it also receives the correct identifier. And the method above is actually an overly simplistic method—many cars have more sophisticated communication between the computer and the key, involving several communications in both directions, even using encrypted communication—making fooling the car's computer even harder. A drawback of secure car keys is that you

 


Figure 3.50 Secure car key FSM. Recall that each edge's condition includes an implicit rising clock edge.

 


Figure 3.51 Secure car key timing diagram.

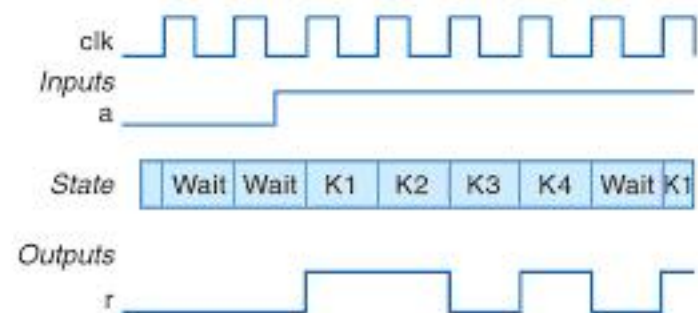


Figure 3.52 Secure car key timing diagram for a different sequence of values on input a .

can't just run down to the local hardware store and copy those keys for \$5 any longer—copying keys requires special tools that today can run \$50-\$100. A common problem while computer chip keys were becoming popular was that low-cost locksmiths didn't realize the keys had chips in them, so copies were made and the car owners went home and later couldn't figure out why their car wouldn't start, even though the key fit in the ignition slot and turned.

Example 3.5 Flight-attendant call button

This example uses an FSM to describe the desired behavior of the flight-attendant call button system from Figure 3.1. The FSM has inputs *Call* and *Cncl* for the call and cancel buttons, and output *L* to control the light. *Call* will be given priority if both buttons are pressed. The FSM has two states, *LightOff*, which sets *L* to 0, and *LightOn*, which sets *L* to 1, as shown in Figure 3.53. *LightOff* is the initial state. The FSM stays in that state until *Call* is 1, which causes a transition to *LightOn*. If *Call* is 0, the FSM stays in *LightOff*. In state *LightOn*, the only way to transition back to *LightOff* is if *Cncl* is 1 and *Call* is 0 (because the call button has priority), meaning $Cncl * Call'$. If that condition is false, i.e., $(Cncl * Call')'$ is true, the FSM stays in *LightOn*.

Notice how clearly the FSM captures the behavior of the flight-attendant call button system. Once you understand FSMs, an FSM description is likely to be more concise and precise than an English description.



Figure 3.53 FSM for flight-attendant call button system.

How to Capture Desired System Behavior as an FSM

The previous section showed FSM examples, but how were those FSMs originally created? Creating an FSM that captures desired system behavior can be a challenging task for a designer. Using the following method can help:

- List states: First list all possible states of the system, giving each a meaningful name, and denoting the initial state. Optionally add some transitions if they help indicate the purpose of each state.
- Create transitions: For each state, define all possible transitions leaving that state.
- Refine the FSM: Execute the FSM mentally and make any needed improvements.

The method described above is just a guide. Capturing behavior as an FSM may require some creativity and trial-and-error, as is the case in some other engineering tasks, like computer programming. For a complex system, a designer may at first list a few states, and then upon defining transitions the designer may decide that more states are required. While creating an FSM, the preciseness of the FSM may cause the designer to realize that the system's behavior should be different than originally anticipated. Note also that many different FSMs could be created that describe the same desired behavior; one FSM may be easier to understand while another FSM may have fewer states, for example. Experience can help greatly in creating correct and easy-to-understand FSMs that capture desired system behavior.

*image
not
available*

the FSM should go to state *Red1*; we'd already added that transition (ar). If a button is pressed and that button is not the red button (ar'), then the FSM should somehow enter a "fail" mode and not unlock the door. At this point, we might consider adding another state called *Fail*. Instead, we decide that the FSM should go back to the *Wait* state and just wait for the start button to be pressed again, so we add such a transition with condition ar' as shown.

The pattern of three transitions for state *Start* can be replicated for states *Red1*, *Blue*, and *Green*, modified to detect the correct colored button press as shown in Figure 3.57. Finally, we must decide what the FSM should do after the FSM reaches state *Red2* and unlocks the door. For simplicity of this example, we decide to have the FSM just return to state *Wait*, which locks the door again; a real system would keep the door unlocked for a fixed period of time before locking it again.

 


Figure 3.57 Code detector FSM with complete transitions.

Refine the FSM: We can now mentally execute the FSM to see if it behaves as desired:

- The FSM begins in the *Wait* state. As long as the start button is not pressed (s'), the FSM stays in *Wait*; when the start button s is pressed (and a rising clock edge arrives, of course), the FSM goes to the *Start* state.
- Being in the *Start* state means the FSM is now ready to detect the sequence red, blue, green, red. If no button is pressed (a'), the FSM stays in *Start*. If a button is pressed AND that button is the red button (ar), the FSM goes to state *Red1*. Instead, if a button is pressed AND that button is not the red button (ar'), the FSM returns to the *Wait* state—note that when in the *Wait* state, further presses of the colored buttons would be ignored, until the start button is pressed again.
- The FSM stays in state *Red1* as long as no button is pressed (a'). If a button is pressed AND that button is blue (ab), the FSM goes to state *Blue*; if that button is not blue (ab'), the FSM returns to state *Wait*. At this point, we detect a potential problem—what if the red button is still being pressed as part of the first button press when the next rising clock edge arrives? The FSM would go to state *Wait*, which is not what we want. One solution is to add another state, *Red1_Release*, that the FSM transitions to after *Red1*, and in which the FSM stays until $a=0$. For simplicity, we'll instead assume that each button has a special circuit that synchronizes the button with the clock signal. That circuit sets its output to 1 for exactly one clock cycle for each unique press of the button. This is necessary to ensure that the current state doesn't inadvertently change to another state if a button press lasts longer than a single clock cycle. We'll design such a synchronization circuit in Example 3.9.
- Likewise, the FSM stays in state *Blue* as long as no button is pressed (a'), and goes to state *Green* on condition ag , and state *Wait* on condition ag' .
- Finally, the FSM stays in *Green* if no button is pressed, and goes to state *Red2* on condition ar , and to state *Wait* on condition ar' .
- If the FSM makes it to state *Red2*, that means that the user pressed the buttons in the correct sequence—*Red2* will set $u=1$, thus unlocking the door. Note that all other states set $u=0$. The FSM then returns to state *Wait*.

The FSM works well for normal button presses, but let's mentally execute the FSM for unusual cases. What happens if the user presses the start button and then presses *all three colored buttons simultaneously*, four times in a row? The way the FSM is defined, the door would unlock! A solution to this undesired situation is to modify the transitions between the states that detect correct colored button presses, to detect not only the correct colored button press, but also

that the other colored buttons are *not* pressed. For example, for the transition leaving state *Start* with condition ar , the condition should instead be $a(rb'g')$. That change also means that the transition going back to state *Wait* should have the condition $a(rb'g')$. The intuitive meaning of that condition is that a button was pressed, but it was not just the red button. Similar changes can be made to the other transition conditions too, resulting in the improved FSM of Figure 3.58.

 


Figure 3.58 Improved code detector FSM.

► 3.4 CONTROLLER DESIGN

Standard Controller Architecture for Implementing an FSM as a Sequential Circuit

The previous section provided examples of capturing sequential behavior using FSMs. This section defines a process to convert an FSM to a sequential circuit. The sequential circuit that implements an FSM is commonly called a **controller**. Converting an FSM to a controller is quite straightforward when a standard pattern, commonly called a standard architecture, is used for the controller. Other ways exist for implementing an FSM, but using the standard architecture results in a straightforward design process.

A standard controller architecture for an FSM consists of a register and combinational logic. For example, the standard controller architecture for the laser timer FSM of Figure 3.45 is shown in Figure 3.59. The controller's register stores the current FSM state and is thus called a **state register**. Each state is represented as a unique bit encoding. For example, the laser timer's *Off* state could be encoded as 00, *On1* as 01, *On2* as 10, and *On3* as 11, the four states thus requiring a 2-bit state register.

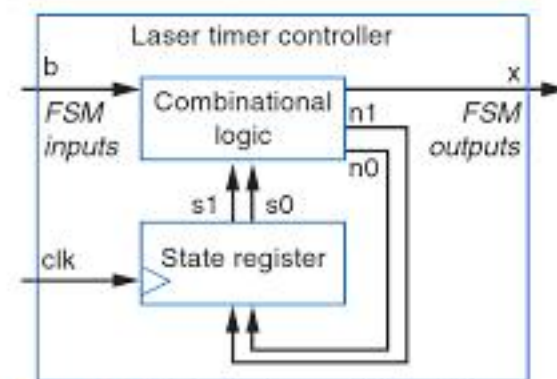


Figure 3.59 Standard controller architecture for the laser timer.

The combinational logic computes the output values for the present state, and also computes the next state based on the current state and current input values. Its inputs are thus the state register bits ($s1$ and $s0$ in the example of Figure 3.59) and the FSM's external inputs (b for the example). The combinational logic's outputs are the outputs of

*image
not
available*

*image
not
available*

We then obtain the sequential circuit in Figure 3.62, implementing the FSM.

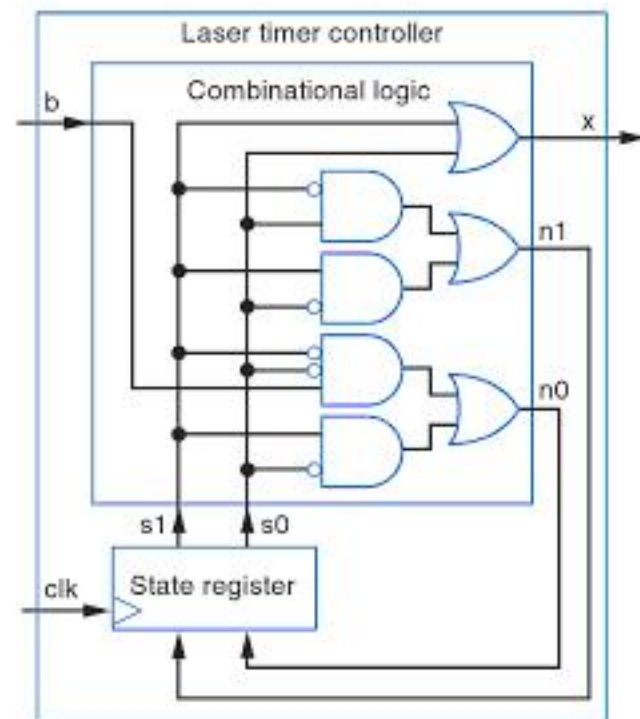


Figure 3.62 Final implementation of the three-cycles-high laser timer controller.

Many textbooks use different table organizations from that in Table 3.3. However, we intentionally organized the table so that it serves both as a *state table*, which is a tabular representation of an FSM, and as a truth table that can be used to design the combinational logic of the controller.

Example 3.8 Understanding the laser timer controller's behavior

To aid in understanding how a controller implements an FSM, this example traces through the behavior of the three-cycles-high laser timer controller. Assume the system is initially in state 00 ($s1s0=00$), b is 0, and the clock is currently low. As shown in Figure 3.63(a), based on the combinational logic, x will be 0 (the desired output in state 00), $n1$ will be 0, and $n0$ will be 0, meaning the value 00 will be waiting at the state register's inputs. Thus, on the *next* clock edge, 00 will be loaded into the state register, meaning the system stays in state 00—which is correct.

Now suppose b becomes 1. As shown in Figure 3.63(b), x will still be 0, as desired. $n1$ will be 0, but $n0$ will be 1, meaning the value 01 will be waiting at the state register's inputs. Thus, on the *next* clock edge, 01 will be loaded into the state register, as desired.

As in Figure 3.63(c), soon after 01 is loaded into the state register, x will become 1 (after the register is loaded, there's a slight delay as the new values for $s1$ and $s0$ propagate through the combinational logic gates). That output is correct—the system should output $x=1$ when in state 01. Also, $n1$ will become 1 and $n0$ will equal 0, meaning the value 10 will be waiting at the state register inputs. Thus, on the next clock edge, 10 will be loaded into the state register, as desired.

After 10 is loaded into the state register, x will stay 1, and $n1n0$ becomes 11. When another clock edge comes, 11 will be loaded into the register, x will stay 1, and $n1n0$ becomes 00.

When another clock edge comes, 00 will be loaded into the register. Soon after, x will become 0, and if b is 0, $n1n0$ will stay 00; if b is 1, $n1n0$ will become 01. Notice that the system is back in the state where it started.

Understanding how a state register and combinational logic implement a state machine can take a while, since in a particular state (indicated by the value presently in the state register), we generate

*image
not
available*

$bo=0$ again, so that bo was 1 for just one cycle, as desired. The FSM goes from B to A if bi returned to 0. If bi is still 1, the FSM goes to state C , where the FSM waits for bi to return 0, causing a transition back to state A .

Step 2A: Set up the architecture. Because the FSM has three states, the architecture has a two-bit state register, as in Figure 3.65(b).

Step 2B: Encode the states. The three states can be straightforwardly encoded as 00, 01, and 10, as in Figure 3.65(c).

Step 2C: Fill in the truth table. We convert the FSM with encoded states to a truth table for the controller's combinational logic, as shown in Figure 3.65(d). For the unused state 11, we have chosen to output $bo=0$ and return to state 00.

Step 2D: Implement the combinational logic. We derive the equations for each combinational logic output, as shown in Figure 3.65(e), and then create the final circuit as shown.

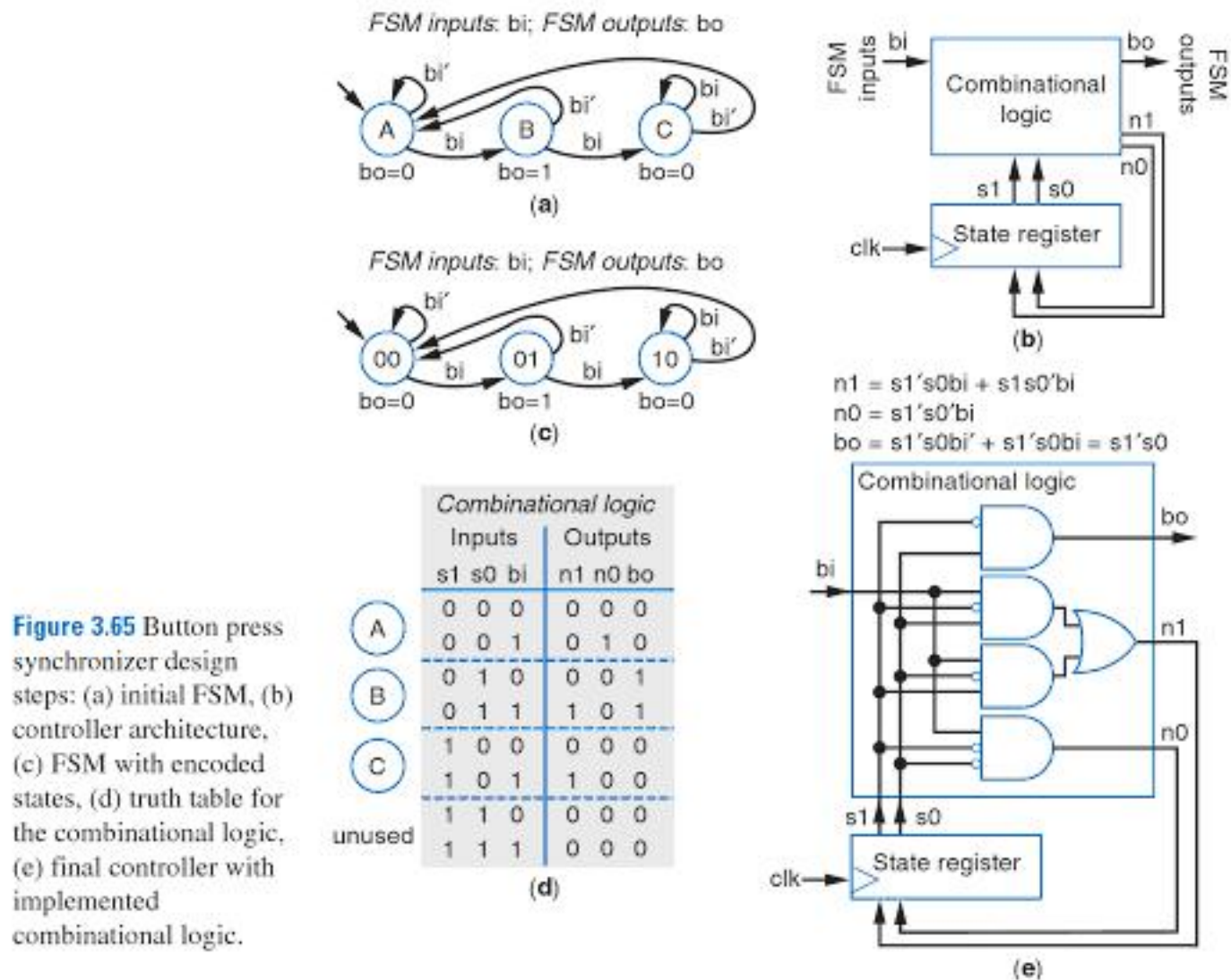


Figure 3.65 Button press synchronizer design steps: (a) initial FSM, (b) controller architecture, (c) FSM with encoded states, (d) truth table for the combinational logic, (e) final controller with implemented combinational logic.

Example 3.10 Sequence generator

This example designs a sequential circuit with four outputs: w , x , y , and z . The circuit should generate the following sequence of output patterns: 0001, 0011, 1100, and 1000, one per clock cycle. After 1000, the circuit should repeat the sequence. Sequence generators are common in a variety of systems, such as a system that blinks a set of four lights in a particular pattern for a festive lights display. Another example is a system that rotates an electric motor a fixed number of degrees each clock cycle by powering magnets around the motor in a specific sequence to attract the magnetized motor to the next position in the rotation—known as a *stepper motor*, because the motor rotates in steps.




The sequence generator controller can be designed using the controller design process:

- Step 1: Capture the FSM.** Figure 3.66 shows an FSM having four states labeled A , B , C , and D (though any other four unique names would do just fine) to generate the desired sequence.
- Step 2A: Set up the architecture.** The standard controller architecture for the sequence generator will have a 2-bit state register to represent the four possible states, no inputs to the logic, and outputs w , x , y , z from the logic, along with outputs $n1$ and $n0$, as shown in Figure 3.67.
- Step 2B: Encode the states.** The states can be encoded as follows— A : 00, B : 01, C : 10, D : 11. Any other encoding with a unique code for each state would also be fine.
- Step 2C: Fill in the truth table.** Table 3.4 shows the table for the FSM with encoded states.
- Step 2D: Implement the combinational logic.** An equation can be derived for each output of the combinational logic directly from the truth table. After some algebraic simplification, the equations are those shown below. The final circuit is shown in Figure 3.68.

TABLE 3.4 State table for sequence generator controller.

	Inputs		Outputs					
	$s1$	$s0$	w	x	y	z	$n1$	$n0$
A	0	0	0	0	0	1	0	1
B	0	1	0	0	1	1	1	0
C	1	0	1	1	0	0	1	1
D	1	1	1	0	0	0	0	0

$$\begin{aligned}
 w &= s1 \\
 x &= s1s0' \\
 y &= s1's0 \\
 z &= s1' \\
 n1 &= s1 \text{ xor } s0 \\
 n0 &= s0'
 \end{aligned}$$

   Figure 3.68 Sequence generator controller with implemented combinational logic.**Figure 3.66** Sequence generator FSM.**Figure 3.67** Sequence generator controller architecture.

Example 3.11 Secure car key controller (continued)

Let's complete the design for the secure car key controller from Example 3.4. We already carried out **Step 1: Capture the FSM**, shown in Figure 3.50. The remaining steps are as follows.

Step 2A: Set up the architecture. The FSM has five states, and thus requires a 3-bit state register, which can represent eight states; three states will be unused. The inputs to the combinational logic are a and the three state bits s_2 , s_1 , and s_0 , while the outputs are signal r and next state outputs n_2 , n_1 , and n_0 . The architecture is shown in Figure 3.69.

Step 2B: Encode the states. Let's encode the states using a straightforward binary encoding of 000 through 100. The FSM with state encodings is shown in Figure 3.70.

Step 2C: Fill in the truth table. The FSM converted to a truth table for the logic is shown in Table 3.5. For the unused states, we have chosen to set $r = 0$ and the next state to 000.

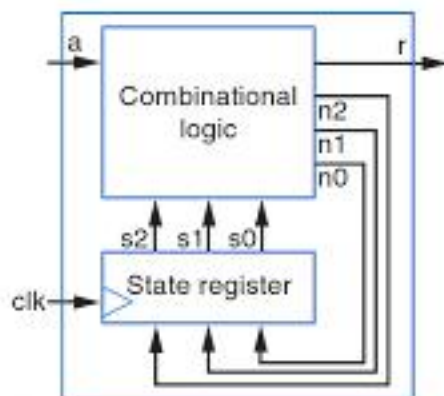


Figure 3.69 Secure car key controller architecture.

 


Figure 3.70 Secure car key FSM with encoded states.

Step 2D: Implement the combinational logic. We can design four circuits, one for each output, to implement the combinational logic. We leave this step as an exercise for the reader.

TABLE 3.5 Truth table for secure car key controller's combinational logic.

	Inputs				Outputs			
	s_2	s_1	s_0	a	r	n_2	n_1	n_0
Wait	0	0	0	0	0	0	0	0
	0	0	0	1	0	0	0	1
K1	0	0	1	0	1	0	1	0
	0	0	1	1	1	0	1	0
K2	0	1	0	0	1	0	1	1
	0	1	0	1	1	0	1	1
K3	0	1	1	0	0	1	0	0
	0	1	1	1	0	1	0	0
K4	1	0	0	0	1	0	0	0
	1	0	0	1	1	0	0	0
Unused	1	0	1	0	0	0	0	0
	1	0	1	1	0	0	0	0
	1	1	0	0	0	0	0	0
	1	1	0	1	0	0	0	0
	1	1	1	0	0	0	0	0
	1	1	1	1	0	0	0	0

Converting a Circuit to an FSM (Reverse Engineering)

We showed in Section 2.6 that a circuit, truth table, and equation were all forms able to represent the same combinational function. Similarly, a circuit, state table, and FSM are all forms able to represent the same sequential function.

The process in Table 3.2 for converting an FSM to a circuit can be applied in reverse to convert a circuit to an FSM. In general, converting a circuit to an equation or FSM is known as *reverse engineering* the behavior of the circuit. Not only is reverse engineering useful to help develop a better understanding of sequential circuit design, but it can also be used to understand the behavior of a previously-designed circuit such as a circuit created by a designer who is no longer at a company, and also to check that a circuit we designed has the correct behavior.

Example 3.12 Converting a sequential circuit to an FSM

Given the sequential circuit in Figure 3.71, find an equivalent FSM. We start from step 2D in Table 3.2. The combinational circuit already exists. Step 2C fills in a truth table. The combinational logic in the controller architecture has three inputs: two inputs s_0 and s_1 represent the contents of the state register, and x is an external input. Thus the truth table will have 8 rows because there are $2^3 = 8$ possible combinations of inputs. After listing the truth table and enumerating all combinations of inputs (e.g., $s_1 s_0 x = 000$, ..., $s_1 s_0 x = 111$), the techniques in Section 2.6 can be used to fill in the values of the outputs. Consider the output y . The combinational circuit shows that $y = s_1'$. Knowing this, we place a 1 in the y column of the truth table in every row where $s_1 = 0$, and place a 0 in the remaining spaces in the y column. Consider n_0 , which the circuit shows as having the Boolean equation $n_0 = s_1' s_0' x$. Accordingly, we set n_0 to 1 when $s_1 = 0$ and $s_0 = 0$ and $x = 1$. We fill in the columns for z and n_1 using a similar analysis and move on to the next step.

Step 2B encodes the states. The states have already been encoded, so this step in reverse assigns a name to encoded state. We arbitrarily choose the names A , B , C , and D , seen in Table 3.6.

Step 2A sets up the standard controller architecture. This step requires no work since the controller architecture was already defined.

Finally, step 1 captures the FSM. Initially, we can set up an FSM diagram with the four states whose names were given in step 2A, shown in Figure 3.72(a). Next, we list the values of the FSM outputs y and z next to each state as defined by the truth table

 


Figure 3.71 Circuit with unknown behavior.

TABLE 3.6 Truth table for circuit.

	Inputs			Outputs			
	s_1	s_0	x	n_1	n_0	y	z
A	0	0	0	0	0	1	0
	0	0	1	0	1	1	0
B	0	1	0	0	0	1	0
	0	1	1	1	0	1	0
C	1	0	0	0	0	0	1
	1	0	1	1	0	0	1
D	1	1	0	0	0	0	0
	1	1	1	0	0	0	0

A designer can verify the above two properties using Boolean algebra. The exclusive transitions property can be verified by ensuring that the *AND of every pair of conditions on a state's transitions always results in 0*. For example, if a state has two transitions, one with condition x and the other with condition $x'y$, transformations of Boolean algebra can be used as follows:

$$\begin{aligned} & x * x'y \\ &= (x * x') * y \\ &= 0 * y \\ &= 0 \end{aligned}$$

If a state has three transitions with conditions $C1$, $C2$, and $C3$, the designer can verify that $C1*C2=0$, $C1*C3=0$, and finally that $C2*C3=0$, thus verifying that every pair yields 0. Note that verifying that $C1*C2*C3=0$ does *not* verify that the transitions are exclusive; for example, if $C1$ and $C2$ were exclusive but $C2$ and $C3$ were not, $C1*C2*C3$ would still equal 0 because $0*C3=0$.

The second property of complete transitions can be verified by checking that the *OR of all the conditions on a state's transitions results in 1*. Considering the same example of a state that has two transitions, one with condition x and the other with condition $x'y$, transformations of Boolean algebra can be applied as follows:

$$\begin{aligned} & x + x'y \\ &= x*(1+y) + x'y \\ &= x + xy + x'y \\ &= x + (x+x')y \\ &= x + y \end{aligned}$$

The OR of those two conditions is not 1 but rather $x+y$. If x and y were both 0, neither condition would be true, and so the next state would not be specified in the FSM. Figure 3.75(b) fixed this problem by adding another transition, $x'y'$. Checking these transitions yields:

$$\begin{aligned} & x + x'y + x'y' \\ &= x + x'(y+y') \\ &= x + x'*1 \\ &= x + x' \\ &= 1 \end{aligned}$$

If a state has three transitions with conditions $C1$, $C2$, and $C3$, the designer can verify that $C1+C2+C3=1$.

Proving the properties for the transitions of every state can be time-consuming. A good FSM capture tool will verify the above two properties automatically and inform the designer of any problems.

*image
not
available*

*image
not
available*

► 3.5 MORE ON FLIP-FLOPS AND CONTROLLERS

Non-Ideal Flip-Flop Behavior

When first learning digital design we assume ideal behavior for logic gates and flip-flops, just like when first learning physics of motion we assume there's no friction or wind resistance. However, there is a non-ideal behavior of flip-flops—metastability—that is such a common problem in the practice of real digital design, we feel obliged to discuss the issue briefly here. Digital designers in practice should study metastability and possible solutions quite thoroughly before doing serious designs. Metastability comes from failing to meet flip-flop setup or hold times, which are now introduced.

Setup Times and Hold Times

Flip-flops are built from wires and logic gates, and wires and logic gates have delays. Thus, a real flip-flop imposes some restrictions on when the flip-flop's inputs can change relative to the clock edge, in order to ensure correct operation despite those delays. Two important restrictions are:

- **Setup time:** The inputs of a flip-flop (e.g., the D input) must be stable for a minimum amount of time, known as the *setup time*, before a clock edge arrives. This intuitively makes sense—the input values must have time to propagate through any flip-flop internal logic and be waiting at the internal gates' inputs before the clock pulse arrives.
- **Hold time:** The inputs of a flip-flop must remain stable for a minimum amount of time, known as the *hold time*, after a clock edge arrives. This also makes intuitive sense—the clock signal must have time to propagate through the internal gates to create a stable feedback situation.

A related restriction is on the minimum clock pulse width—the pulse must be wide enough to ensure that the correct values propagate through the internal logic and create a stable feedback situation.

A flip-flop typically comes with a datasheet describing setup times, hold times, and minimum clock pulse widths. A **datasheet** is a document that tells a designer what a component does and how to properly use that component.

Figure 3.80 illustrates an example of a setup time violation. D changed to 0 too close to the rising clock. The result is that R was not 1 long enough to create a stable feedback situation in the cross-coupled NOR gates with Q being 0. Instead, Q glitches to 0 briefly. That glitch feeds back to the top NOR gate, causing Q' to glitch to 1 briefly. That glitch feeds back to the bottom NOR gate, and so on. The oscillation would likely continue until a race condition caused the circuit to settle into a stable situation of Q = 0 or Q = 1—or the circuit could enter a metastable state, which we now describe.

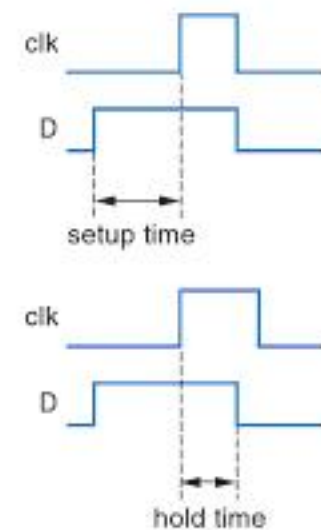


Figure 3.79 Flip-flop setup and hold time restrictions.

*image
not
available*

*image
not
available*

*image
not
available*

*image
not
available*

image

not

available

570 ▶ Index

Event [107](#), 167
 event (in VHDL) 502
 Exact algorithm 339
 Excitation table [120](#)
 Exclusive (transitions) 142
 Exclusive OR 81
 Execute 466
 Expand operation 346
 Expanding (a term) 340
 Expression 62

F

Fabrication plant (fab) 415
 Factoring 350
 Fahrenheit 213
 Falling edge-triggered flip-flop [116](#)
 Fanout 225
 Feature size 449
 Field programmable gate array 424
 FIFO (first-in first-out) 300
 FIFO queue 300
 Filter 278
 Filtering 313
 Finite Impulse Response filter 276
 Finite-state automata [126](#)
 Finite-state machine 124, [126](#), 505
 FIR filter 276, 313, 384, 391
 FIR filter (pipelined) 379
 First-in first-out (FIFO) 300
 Fixed-point arithmetic 550
 Flash memory 296
 Floating point number 552
 Flop [116](#)
 Flow-of-control instruction 480
 FPGA 424, 445, 446, 448
 Frame 393
 Frame (video) 267
 Frequency 117
 FSM 124, [126](#)
 FSM with data 253
 FSMD 253
 Full-adder 184
 Full-custom IC 414
 Full-subtractor 197
 Function cover 340
 Functions (of a register) 175
 Fuse-based PLD 441
 Fuse-based ROM 294

G

GAL (generic array logic) 444
 Gate 46
 Gate (of a transistor) 41
 Gate array 424
 Gate array ASIC 417, 448

Gate delay 91
 Gated D latch [112](#)
 Gated SR latch [111](#)
 Gbyte 21
 General-purpose computer [4](#)
 General-purpose processor 461
 Generate 370
 Generic array logic (GAL) 444
 Gigabyte 21
 Glitching 151
 Global register 303
 Global signal 303
 Google [12](#)
 Ground 36, 439

H

Haitz's Law 453
 Half-adder 184, 190, 417
 Hard core 452
 Hardware description language (HDL) 489
 HDL x, 95, 489
 Hertz 118, 278
 Heuristic 339
 Hex [16](#)
 Hexadecimal [16](#)
 Hierarchical carry-lookahead adder 374
 Hierarchy 305
 High-level state machine 248
 HLSM 248
 Hold time [146](#)
 Hz (Hertz) 118

I

IC 39, 40, 413
 IC capacity 448
 IC type 413
 Idempotent 541
 Idempotent law 58
 Identity comparator 191
 Identity element 538
 Identity property [56](#)
 If-then statement 282
 If-then-else statement 282
 Implicant 340
 Implication table 353
 Increment 215
 Incrementer 190
 Indirect addressing 480
 initial procedure (in Verilog) 499
 Initial state [126](#), 150
 Input (in Verilog) 491
 Instance 259
 Instantiate 259
 Instruction memory 465
 Instruction register 466

image

not

available

image
not
available

image
not
available

574 ▶ Index

Sensitive (in Verilog) 496
 Sensitive (in VHDL) 495
 sensitive_pos (in SystemC) 503
 Sensitivity list (in Verilog) 496, 504
 Sensitivity list (in VHDL) 495, 504
 Sensor 9
 Sequential circuit 35
 Sequential multiplier 375
 Serial 386
 Serial communication 175, 179
 Serializing 383
 Servant [114](#)
 Set (a latch) [109](#)
 Set (flip-flop input) 149
 Setup time [146](#)
 Seven-segment display [72](#)
 Shannon, Claude 45
 Shared bus 227
 Shift 210
 Shift register 173, 436
 Shifter 211, 214, 259
 Shifting (a register) 173
 Shifts and adds 212
 Shockley, William 38
 SHR (in VHDL) 519
 Sign bit 202
 Signal (in VHDL) 490
 Signed number 202, 212
 Signed-magnitude representation 200
 Significand 552
 Silicon [40](#), [42](#)
 Silicon dioxide 41
 Silicon Valley 42
 Simple PLD 444
 Simulation [94](#)
 Simulator [94](#)
 Single precision 552
 Single-purpose processor 461
 Size 326
 Sliding average 211
 Small-scale integration 439
 SOC 450
 Soda machine dispenser 248
 Soft core (on an FPGA) 451
 Software 22
 Solid state 39
 Source (of a transistor) 41
 Spin (in IC fabrication) 415
 SPLD 444
 Spurious value 187
 SRAM 288
 SSI 39
 SSI chip 439
 Stable [108](#)
 Stage (of a pipeline) 378

Stages 466
 Standard architecture (for sequential circuit) [132](#)
 Standard cell ASIC 416, 448
 Standard representation [68](#)
 State [122](#)
 State diagram 124
 State encoding 354
 State minimization 351
 State reduction 351
 State register [132](#), [168](#), [505](#)
 State table [135](#)
 Static 289
 Static RAM 288
 std_logic (in VHDL) 489
 std_logic_1164 (in VHDL) 489
 std_logic_arith (in VHDL) 517
 std_logic_unsigned (in VHDL) 517
 std_logic_vector (in VHDL) 501
 Stepper motor [138](#)
 Store operation 463
 Storing (in a register) 168
 Storing a bit [106](#)
 Stream 275
 Structure 489
 Structured ASIC 418, 446
 Subtraction method [16](#)
 Subtractor 196
 Sum 53
 Sum of absolute differences (SAD) 281
 Sum of minterms 71
 Sum-of-absolute differences (SAD) 267
 Sum-of-minterms 69, 340
 Sum-of-products 55, 69, 74, 327, 422
 Superscalar processor 482
 Switch 36
 Switch matrix 432
 Switching algebra 537, 538
 Synchronized processors 304
 Synchronous circuit 117
 Synchronous clear 180, 216
 Synchronous reset 150
 Synchronous set 150, 180
 Synthesis 282
 System-on-a-chip (SOC) 450

T

T flip-flop [120](#)
 Tabular method 341
 Tap (in FIR filter) 314
 Tbyte 21
 Technology mapping 417, 427
 Telephone [8](#)
 Terabyte 21
 Term 55
 Terminal count 215

image

not

available